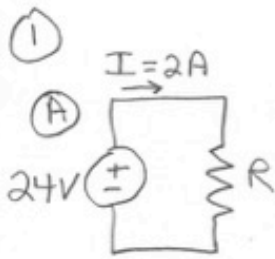


Homework 1 - Answers



Ⓐ $R = \frac{24V}{2A} = 12\Omega$ Ⓑ $I^2 R = 48W$

Ⓒ YES Ⓓ NO Ⓔ $-48W$ Ⓕ $60 \times 48 = 2880J$

② Ⓐ circuit redrawn

Ⓑ $V_1 = 0V$, ground

Ⓒ 200Ω in parallel with $300\Omega =$

$$\frac{200 \times 300}{200 + 300} = 120\Omega$$


$$V_2 = \frac{120}{120 + 80} 10V = 6V$$

Ⓓ $V_3 = 10V$

Ⓔ $I = \frac{10V}{120\Omega + 80\Omega} = 50mA$

3.

A.

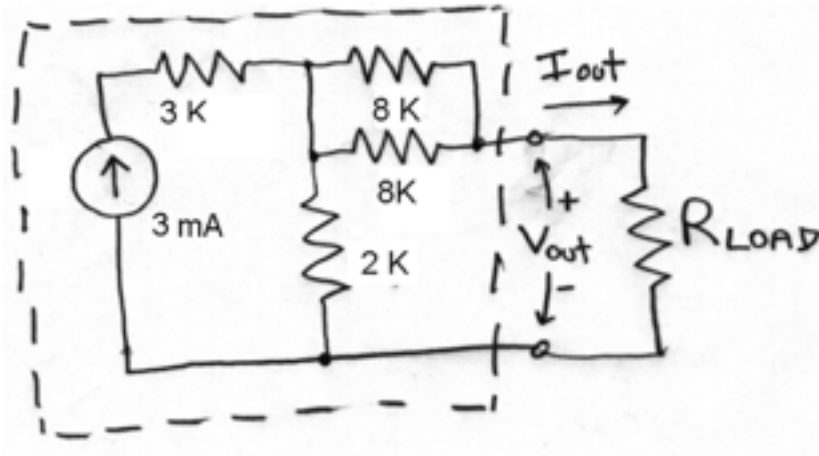

B. Since R_1 is the only component in series with a current source, all of that current must pass through it by Kirchoff's Current Law, that is, 3 mA.

C. R_{LOAD} should be set to 0Ω .

D. R_2 in parallel with R_3 is $4 \text{ K}\Omega$, which with R_4 form a current divider in which $1/3$ of the current will constitute I_{OUT} . Therefore, $I_{NORTON} = 1 \text{ mA}$.

E. R_{LOAD} should be set to $\infty \Omega$.


F. Since $R_{LOAD} = \infty \Omega$, no current will pass through R_2 or R_3 , meaning there will be no voltage drop across them. All of I will pass through R_4 , so $V_{OUT} = V_{THEVENIN} = 3 \text{ mA} \times 2 \text{ K}\Omega = 6 \text{ V}$.

G. $R_{THEVENIN} = R_{NORTON} = V_{THEVENIN} / I_{NORTON} = 6 \text{ V} / 1 \text{ mA} = 6 \text{ K}\Omega$.

H. Since $I = 0$, no current will pass through R_1 . Thus $R_{THEVENIN} = R_{NORTON}$ is R_2 in parallel with R_3 ($4 \text{ K}\Omega$) in series with R_4 ($2 \text{ K}\Omega$), or $6 \text{ K}\Omega$.

4.

A.

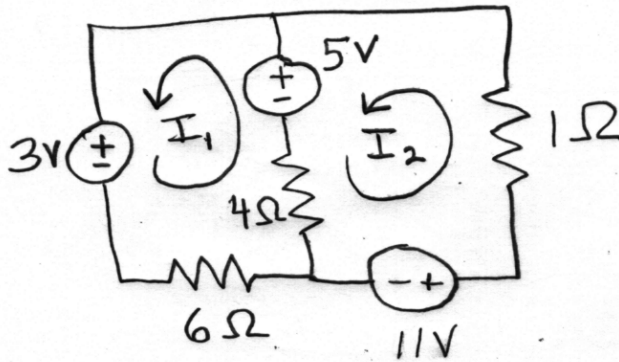

B.

$$10I_1 - 4I_2 = 2$$

$$-4I_1 + 5I_2 = 6$$

C. $I_1 = 1$ A and $I_2 = 2$ A.D. $10(1) - 4(2) = 2$
 $-4(1) + 5(2) = 6$