
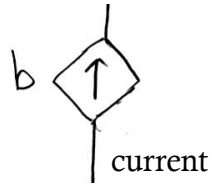


Variable Sources

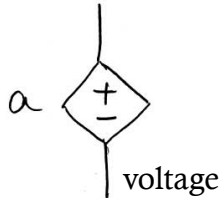

a and b are variables in algebraic expressions.


Example: By Ohm's law,
voltage across resistor,

$$V = IR = 20a$$

By Kirchoff's
voltage law,

$$30 = 20a + 10a$$

Therefore $a = 1A$

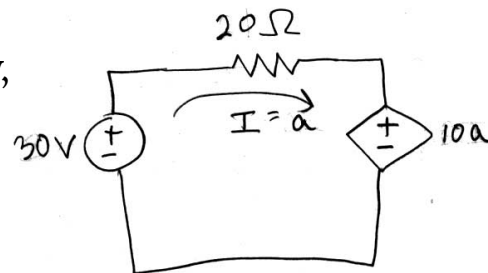

conversion of
units implied




32

Potentiometer – “Pot”



Three-terminal device:
fixed resistor with a
movable wiper.

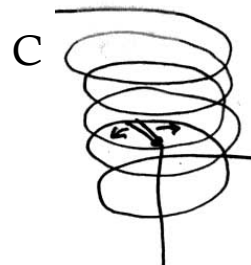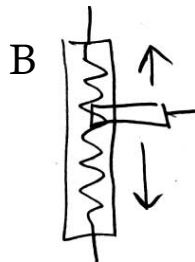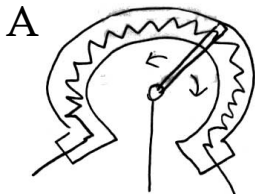
Physically: (A) single-turn wiper on a circular resistor, (B) linear wiper on straight resistor, (C) multi turn wiper on spiral resistor (very accurate).



33


Potentiometer – “Pot”

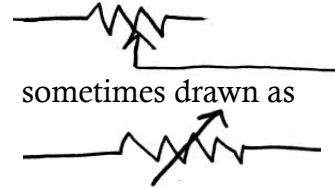- Ignore one lead and you have a simple two-lead variable resistor.



- Typical use: producing a variable fraction of voltage source V_S ; pot provides both resistors of a voltage divider with output between 0 and V_S .

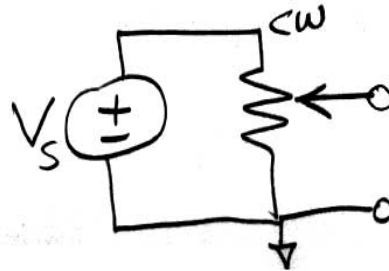“cw” wiper at this end when turned clockwise




34

What to Ignore...

- Estimate the total resistance:



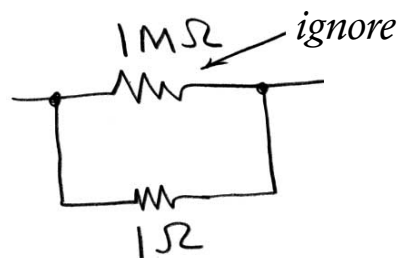Resistors in *series*:
much smaller resistor is essentially a “short circuit” or piece of wire. $\sim 1\text{M}\Omega$



Resistors in *parallel*:
much larger resistor is essentially a “open circuit” or insulator. $\sim 1\Omega$

- Keep tolerance of resistors in mind (e.g. 5%).

35

Resistivity of materials

- A resistor consists of a material with a shape.

assume a cylinder
length L , area A



$$R = \rho \frac{L}{A}$$

- Resistivity* ρ in ohm-meters

insulator (glass, quartz)	10^{16} - 10^{10} Ω M
semi-conductor (silicon)	10^3 - 10^{-5} Ω M
conductors (metal)	10^{-6} - 10^{-8} Ω M
superconductor	0 Ω M
- Conductivity* $\sigma \equiv \frac{1}{\rho}$

36

Resistor Color Code

1st Digit	2nd Digit	3rd Digit
0	0	x1
1	1	x10
2	2	x100
3	3	x10 ³
4	4	x10 ⁴
5	5	x10 ⁵
6	6	x10 ⁶
7	7	x10 ⁷
8	8	x10 ⁸
9	9	x10 ⁹


4th Band - Tolerance		
10% Silver	1% Gold	0.5% Green
5% Gold	2% Red	0.25% Blue

Disk Capacitors Labeling

- 3 digits "ABC" = $AB \times 10^C$ pF
(AB plus C zeros)
- Examples
 - "682" = 6800 pF
 - "104" = 100,000 pF = 0.1 μ F

37

Examples

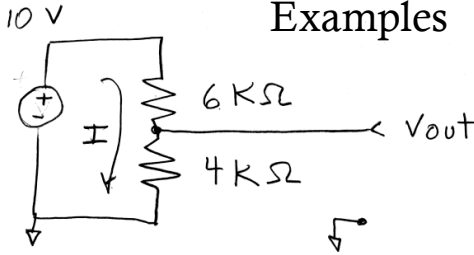

Voltage
"Divider"


Same I through both resistors
total resistance $10\text{K}\Omega$

$$I = \frac{10\text{V}}{10\text{K}\Omega} = 1\text{ma}$$

$$V_{\text{out}} = 1\text{ma} \cdot 4\text{K}\Omega = 4\text{V}$$

leaves 6V across top resistor
Voltage across each resistor proportional
to its resistance.

38

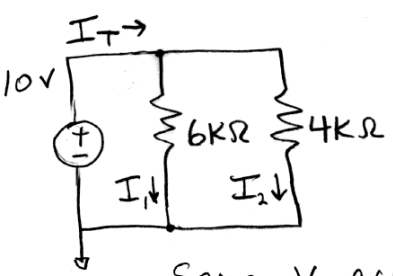

Parallel
Resistors

Same V across both resistors


$$I_1 = 10\text{V} / 6\text{K}\Omega = 1.66\text{ ma}$$

$$I_2 = 10\text{V} / 4\text{K}\Omega = 2.5\text{ ma}$$

$$I_T = 4.16$$

39

Real Voltage Source

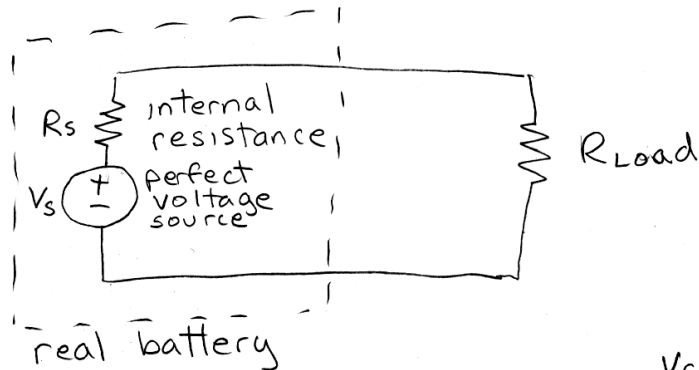

limits maximum current to $\frac{V_s}{R_s}$
 when load = 0Ω
 car batteries have low internal
 resistance, can "source" 10's of "amps"
 expected battery life rated in "ampere hours"
 multiply by voltage to get total energy

40

Real Voltage Source

Other examples of voltage sources

electromagnetic generators

photo voltaic solar cells

Fuel cells

friction ("static" electricity,
lightening)

Nernst equation (ionic gradients)

others?


any case where $R_s \ll R_{Load}$

open faucet – nearly constant pressure

41

Real Current Source

Real current source

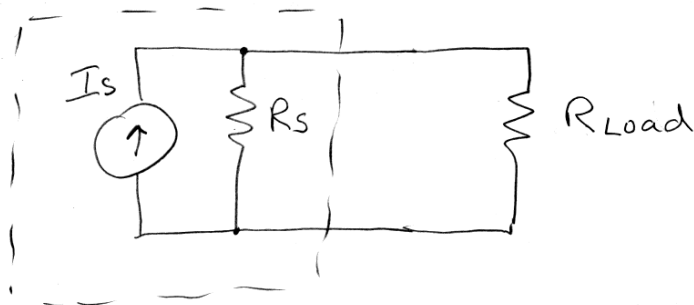

Limits maximum voltage to $I_s R_s$
when $R_{Load} = \infty \Omega$

42

Real Current Source

Examples

Radio antenna


transistors

or any case where $R_s \gg R_{Load}$

dripping faucet – nearly constant flow

43

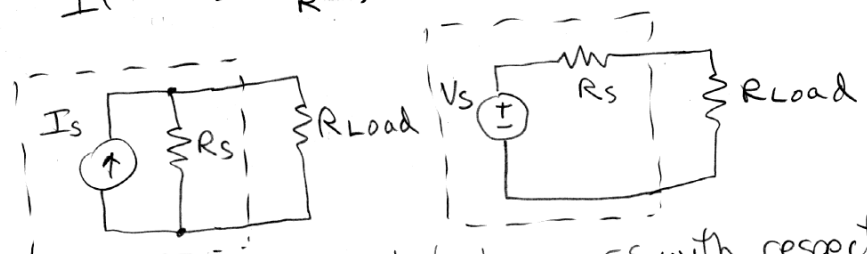IF $I_s = \frac{V_s}{R_s}$, then the two models



have identical behaviors with respect to R_{Load} :


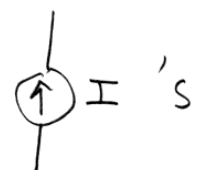

	R_{Load}	I_{Load}	V_{Load}
"short circuit"	0Ω	I_s	$0V$
"open circuit"	$\infty \Omega$	$0A$	V_s

called *Thevenin* and *Norton* equivalents


44

Thevenin Equivalent

ANY NETWORK OF

 's ,  's
 and
 's


can be redrawn as

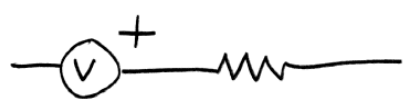

15

Norton Equivalent

ANY NETWORK OF

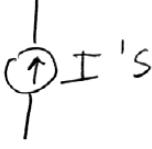resistors 's,  I's

and  V's

Can be rewritten as





46

Superposition Theorem

Superposition Theorem: The current in a branch = sum of currents produced by each source with the other sources set to ϕ

"set to ϕ " means


 \rightarrow short circuit $V=0$

 \rightarrow open circuit $I=0$


47

Superposition Theorem


Example (Scherz p 75)

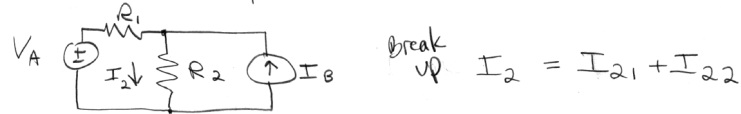

setting $I_B = 0$ (open circuit)

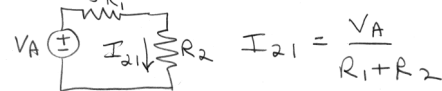

Setting $V_A = 0$ (short circuit)

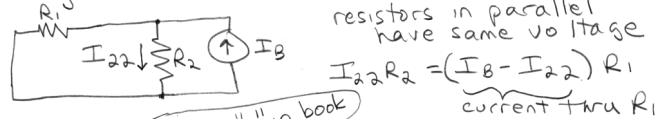

resistors in parallel have same voltage

$$I_{22} R_2 = (I_B - I_{22}) R_1$$

current thru R_1

this is "in" book wrong!!

$$I_{22} = \frac{I_B R_1}{R_1 + R_2}$$

$$I_2 = I_{21} + I_{22} = \frac{V_A + I_B R_1}{R_1 + R_2}$$

↑
this known as the "current divider eq."


Continuing the example, solve for I_1 thru R_1

setting $I_B = 0$



$$I_{11} = \frac{V_A}{R_1 + R_2}$$

Setting $V_A = 0$

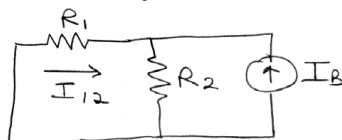

$$-I_{12} R_1 = (I_B + I_{12}) R_2$$

current thru R_2

↑
notice "-" because current is actually going the other way

$$I_{12} = \frac{-I_B R_2}{R_1 + R_2}$$

$$I_1 = \frac{V_A - I_B R_2}{R_1 + R_2}$$