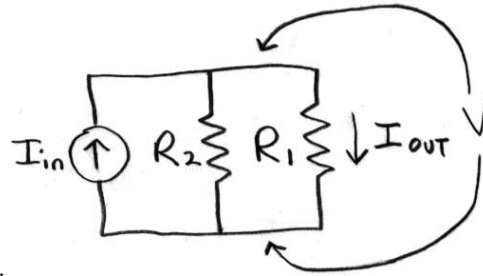


Current Divider

- View as “system” with current input and output.
- Same *voltage* across both resistors.
- Current through each resistor is proportional to its *conductance*.

$$I_{\text{in}} = V(G_1 + G_2)$$

$$I_{\text{out}} = VG_1 = \frac{R_2}{R_1 + R_2} I_{\text{in}}$$



44

If $I_s = \frac{V_s}{R_s}$, then the two models






to R_{Load} : have identical behaviors with respect

	R_{Load}	I_{Load}	V_{Load}
"short circuit"	0Ω	I_s	$0V$
"open circuit"	$\infty \Omega$	$0A$	V_s

called *Thevenin* and *Norton* equivalents

45

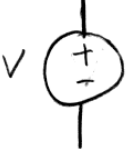


Thevenin Equivalent


ANY NETWORK OF
 's ,  I 's
 and
 V 's
 can be redrawn as



46

Norton Equivalent

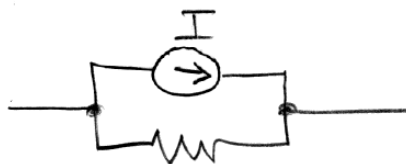
ANY NETWORK OF
 's ,  I 's
 and
 V 's
 can be rewritten as



47

Thevenin Equivalent - Example

What is current through R_3 ?

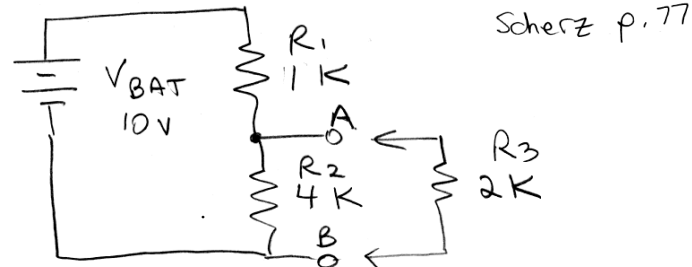

- Find V_{THEV} of “branch” (2-node component)
 - Compute voltage between A and B without R_3 .

$$V_{\text{THEV}} = V_{\text{BAT}} \frac{4\text{K}}{1\text{K} + 4\text{K}} = 8\text{V}$$


48

(continued....)

- Find R_{THEV} of branch
 - Set all sources to zero.

\oplus → short circuit
0V


\oplus → open circuit
0A

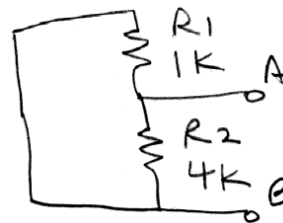

just parallel resistors

$$R_{\text{THEV}} = \frac{R_1 R_2}{R_1 + R_2} = 800\Omega$$

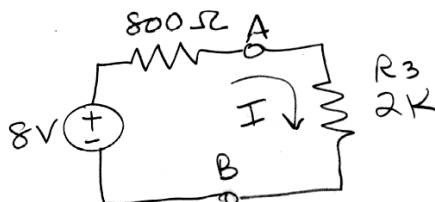
- Now use Thevenin Equivalent to find I through R_3 .



$$I = \frac{8\text{V}}{2\text{K} + 800\Omega} \approx 3\text{mA}$$


49

Norton Equivalent - Example

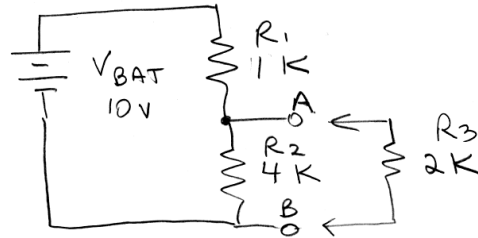

Again, what is current through R_3 ?

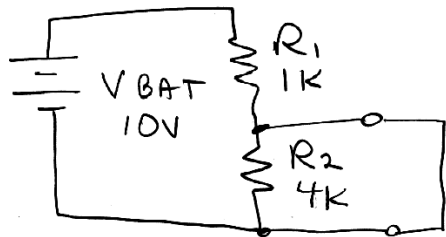- Find I_{NORT} of “branch” (2-node component)
 - Replace R_3 with short-circuit between A and B.



$$I_{NORT} = \frac{10V}{1K} = 10mA$$


50

(continued....)

- Find R_{NORT} the same way as before ($R_{NORT} = R_{THEV}$)

⊕ → short circuit
OV


⊕ → open circuit
OA

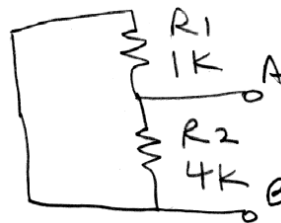

parallel resistors

$$R_{THEV} = \frac{R_1 R_2}{R_1 + R_2} = 800\Omega$$

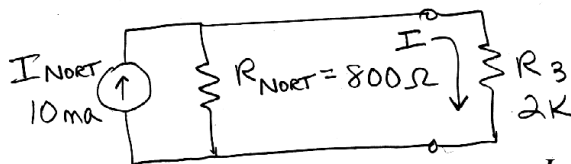- Now use Norton Equivalent to find I through R_3 .



Use the current divider equation


$$I = I_{NORT} \frac{R_{NORT}}{R_3 + R_{NORT}} \cong 3mA$$

51

Superposition Theorem


Superposition Theorem: The current in a branch = sum of currents produced by each source with the other sources set to ϕ

"set to ϕ " means

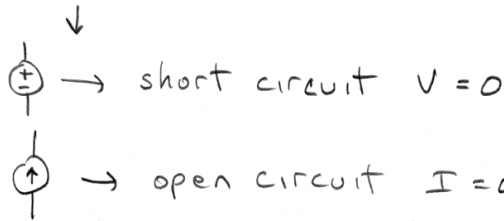


Superposition Theorem


Example (Scherz p 75)

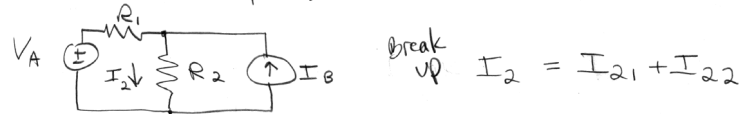

setting $I_B = 0$ (open circuit)

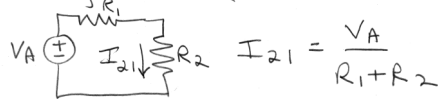

Setting $V_A = 0$ (short circuit)

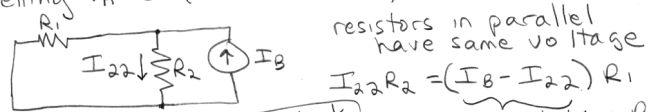

This is "wrong" in book

$$I_{22} = \frac{I_B R_1}{R_1 + R_2}$$

$$I_2 = I_{21} + I_{22} = \frac{V_A + I_B R_1}{R_1 + R_2}$$

This known as the "current divider eq"


continuing the example, solve for I_1
thru R_1

setting $I_B = 0$



$$I_{11} = \frac{V_A}{R_1 + R_2}$$

Setting $V_A = 0$

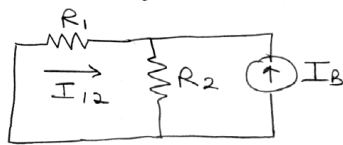

$-I_{12}R_1 = \underbrace{(I_B + I_{12})R_2}_{\text{current thru } R_2}$
notice "-"
because
current is actually
going the other way


$$I_{12} = \frac{-I_B R_2}{R_1 + R_2}$$

$$I_1 = \frac{V_A - I_B R_2}{R_1 + R_2}$$

54

Norton Equiv. by Superposition

Find Norton equivalent with I_{NORT} from a to b .

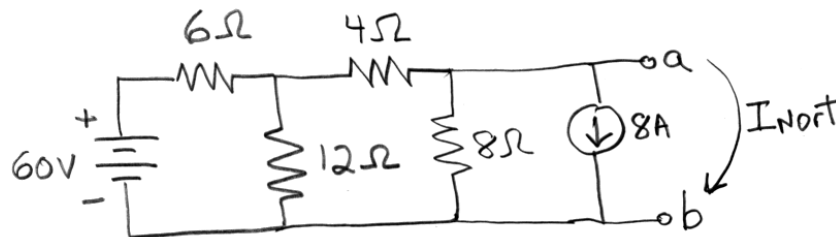


Schaum 5.39

Use superposition to find I_{Nort} , the current
from a to b with a shorted to b


55

(continued....)

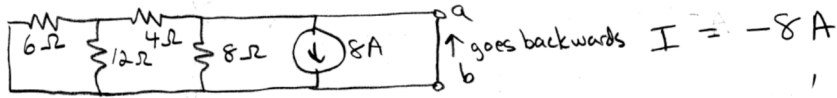- (1) Contribution from current source with battery at 0V (shorted).
Ignore all resistors since all current goes through short from a to b .



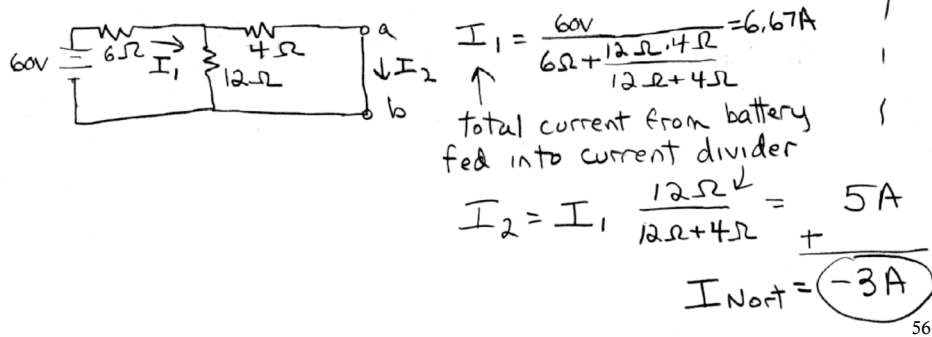
- (2) Contribution from battery with current source at 0A (open).
Ignore 8Ω resistor since it is parallel to short from a to b .



56


(continued....)

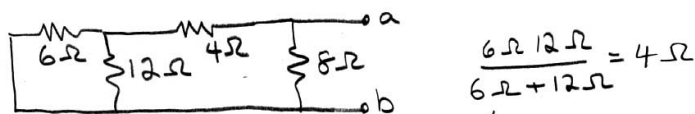R_{Nort} is resistance between a and b with all sources 0.



$$\frac{6\Omega \cdot 12\Omega}{6\Omega + 12\Omega} = 4\Omega$$

← simplify parallel resistors

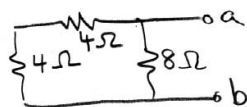


$$R_{Nort} = \frac{8\Omega \cdot 8\Omega}{8\Omega + 8\Omega} = 4\Omega$$

57


Mesh analysis yield simultaneous linear equations.

mesh

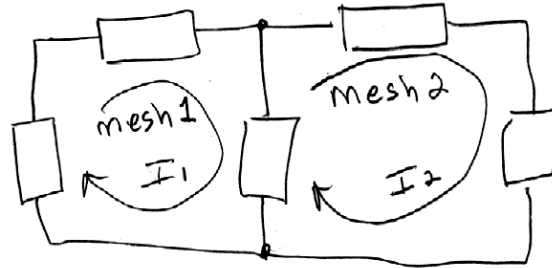

58

Example of a Mesh

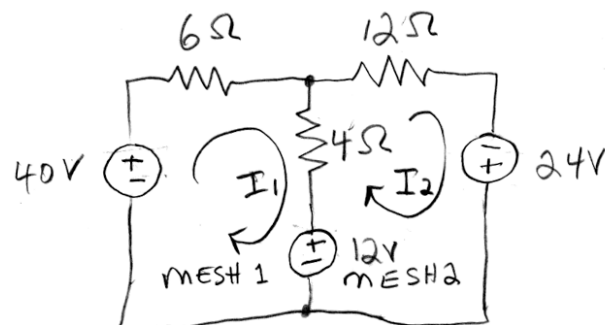


USING KIRCHHOFF'S VOLTAGE LAW

$$10 I_1 - 4 I_2 = 28$$

$$-4 I_1 + 16 I_2 = 36$$

59

Wheatstone Bridge

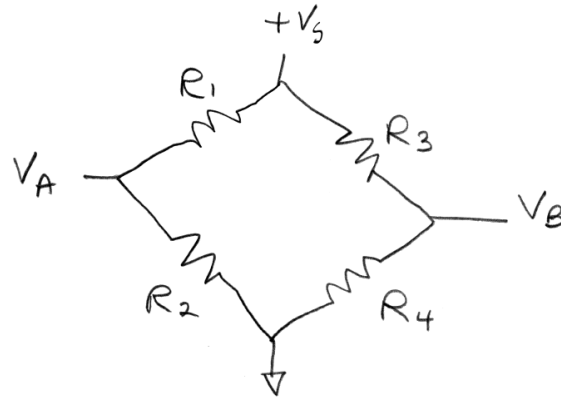

$$V_A = V_B \text{ when } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

basically 2 voltage dividers

60

Wheatstone Bridge

accurate measurement setup
independent of V_s



adjust
pot so
as to
"zero"
the
voltmeter

61

classic galvanometer G

tiny current ($50 \mu\text{A}$)
through coil
moves needle
coil has $\approx 0 \Omega$ resistance


your meter
↓
 R_s is big, $1\text{m}\Omega - 1\text{g}\Omega$
("s" for series)

voltmeter V what's inside

ammeter A R_p is small $< 1 \Omega$
("p" for parallel
Easy to destroy meter!!)


ohmmeter Ω R_o used to adjust
offset.
injects current...
only use on isolated,
non-powered resistors.

62

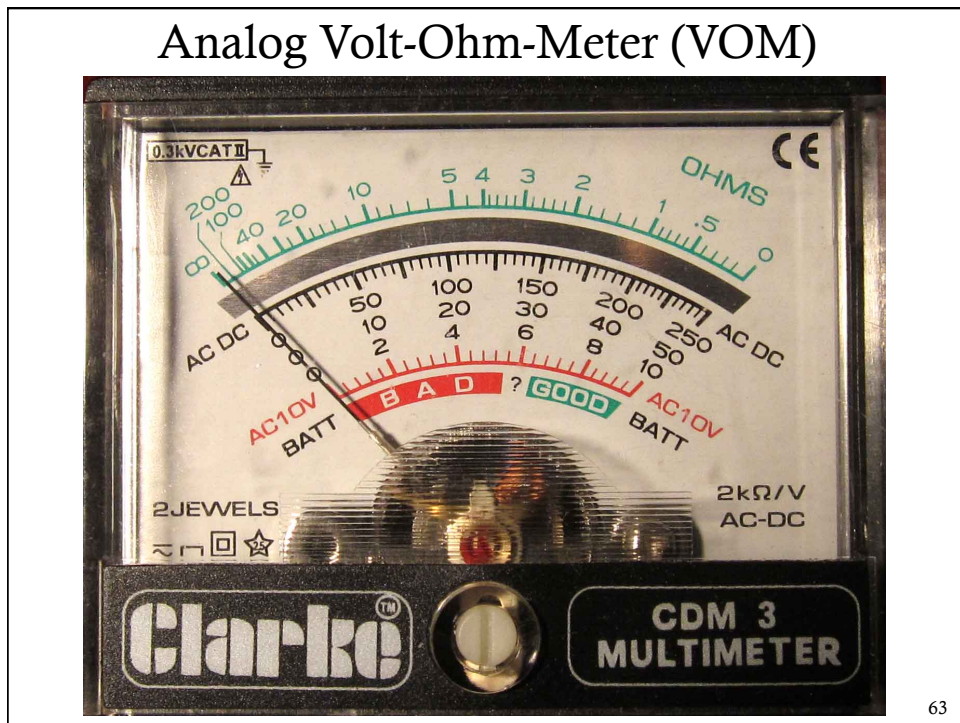

DC Circuits without solutions

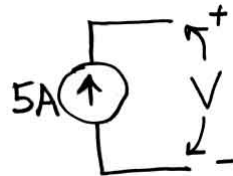- There are basically 2 illegal DC circuits
 - Current source with open circuit: $V = \infty$



- Voltage source with short circuit: $I = \infty$

