

# Electronics is cool

- Electronics has produced the most complex artificial systems in the known universe.
- Only biological systems are more complex, and among them, electrical (nervous) systems are the most complex and miraculous.
- Electronics can go blindingly fast (electrons in wires much lighter, more mobile, and more densely packed than ions in axons).
- You can build your own, cheap!
- You can learn a lot about math by understanding circuits, and a lot about the scientific method by debugging them.

# Section 1 - DC

- DC stands for “Direct Current”  
(though you often hear “DC Voltage.”)
- Time-invariant
- Constant currents
- Constant voltages
- Resistors
- Linear (not differential) equations

# Physical Quantities & Units

physical quantity = numerical value  $\times$  unit

↑  
normally shown in *italics*

<u>Physical Quantity</u>	<u>Unit</u>
“ <i>Q</i> ” charge	C coulomb
“ <i>I</i> ” current	A ampere (amp)


$$6.241 \times 10^{18} \text{ electrons} = -1\text{C}$$

↑  
thank you, Benjamin Franklin

$$1\text{A} = \frac{1\text{C}}{1\text{sec}}, \quad I = \frac{Q}{t}$$

charge, like gallons  
current, like gallons per second


# Water Analogy

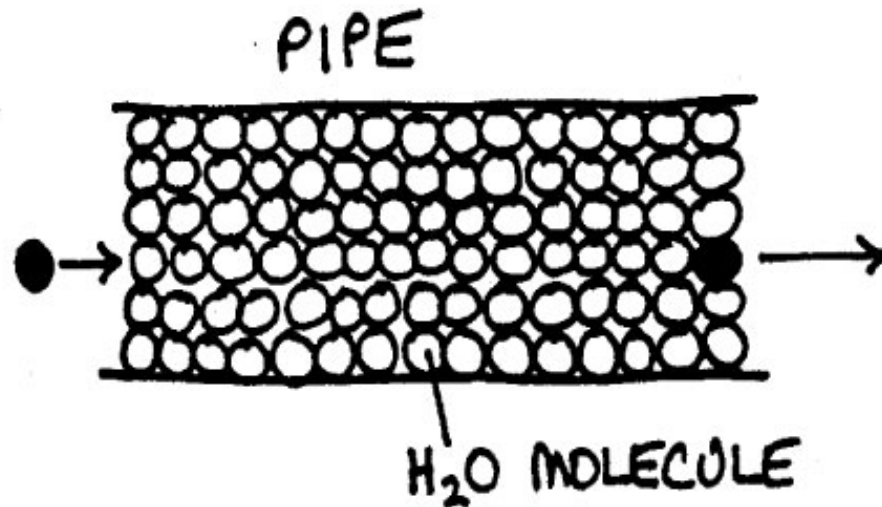

- Practically non-compressible; push one H<sub>2</sub>O molecule in one end of steel pipe and one pops out the other end.
- Flow (current) limited by *viscosity & turbulence*.
- Pressure wave travels at  $\sim$  the speed of *sound*.
- Flow roughly proportional to *pressure*.




Electrons somewhat  
analogous

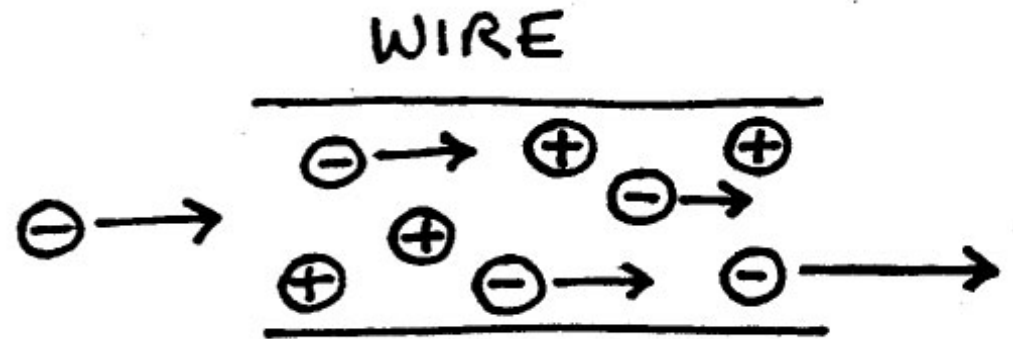

- Practically non-compressible - Nature really hates any buildup of *charge* in a small space.
- Flow (current) limited by *resistance* – bumping into atoms, not linear acceleration as in a vacuum, more like terminal velocity.
- Electric wave travels at  $\sim$  the speed of *light*.
- Flow roughly proportional to *voltage* – roughly equivalent to “electrical pressure”.
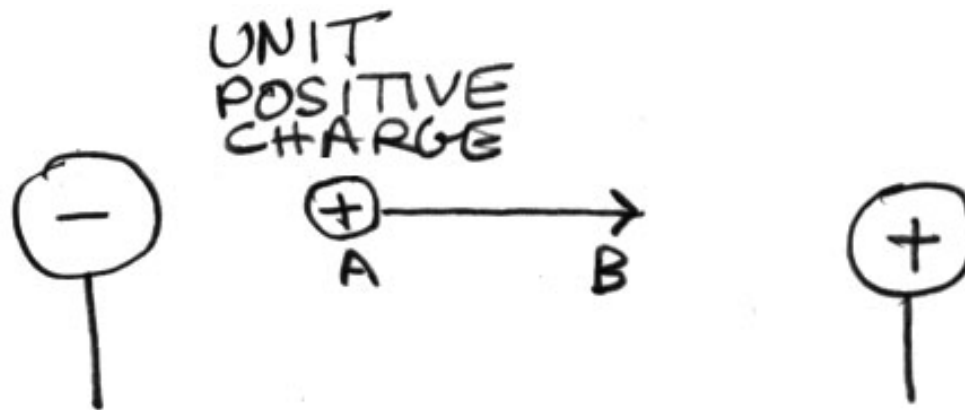
# What is Voltage, really?


- Sometimes called *electromotive force* (EMF) (not really a force) or *potential* (but not potential energy, though it does have to do with energy)
- The voltage difference between points A and B is the energy required to move a unit positive charge (along any path) from A to B.



- Moving from B to A yields the same voltage difference with an opposite sign.
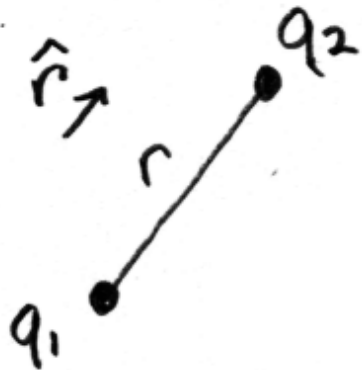
# Electric Field: force on a unit test charge


- Force between two charges,  $q_1$  and  $q_2$



$$\vec{F} = k \frac{q_1 q_2}{r^2} \hat{r}$$

“^” means unit vector

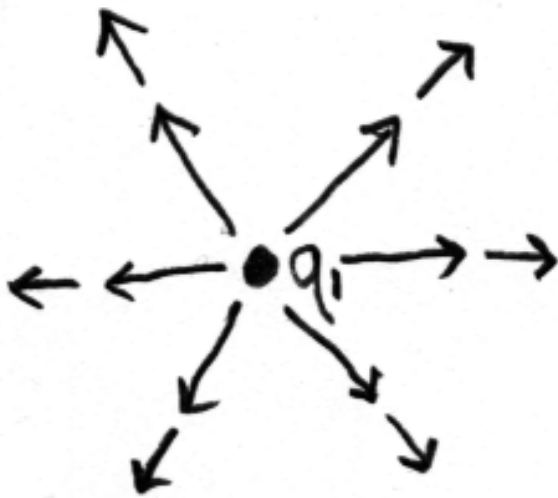- Electric field from a single charge  $q_1$



$$\vec{E} = \frac{\vec{F}}{q_2}$$

Force on a test charge  $q_2$  placed anywhere (normalized to a unit test charge)

# Voltage is the integral of Electric Field

- Voltage between points A and B

$$V(A, B) = - \int_A^B \vec{E} \cdot d\vec{s}$$

Energy (force  $\times$  distance) per unit test charge required to move from point A to B along unit steps  $d\vec{s}$  in path through field  $\vec{E}$ .

- Electric field is (negative) gradient of Voltage.

$$\vec{E} = - \nabla V$$

Electric field  $\vec{E}$  is vector.

Voltage is scalar.

(Note potential confusion between electric field  $\vec{E}$  and energy  $E$ , a scalar)

- Voltage is energy per unit charge.
- In circuits, think about voltage as the pressure *difference* between two points, though voltage is technically not pressure.
- A single point can be said to have a voltage only relative to some reference point, often called the “circuit ground”.
- Power is the brightness of the light bulb; energy is how much gas is in the tank of the generator.
- Power is energy per unit time.
- Power is voltage  $\times$  current (think force  $\times$  distance, though not exactly analogous dimensionally).

## Physical Quantity

## Unit

“ $F$ ” force

N newton

“ $E$ ” energy or “ $W$ ” work

J joule

“ $V$ ” voltage

V volt

“ $P$ ” power

W watt



$$1\text{J (joule)} = 1\text{N (newton)} \times 1\text{M (meter)}$$

$$1\text{V (volt)} = 1\text{J (joule)} / 1\text{C (coulomb)}$$

$$1\text{W (watt)} = 1\text{V (volt)} \times 1\text{A (amp)} = \frac{1\text{J}}{1\text{C}} \times \frac{1\text{C}}{1\text{ sec}} = \frac{1\text{J}}{1\text{ sec}}$$


- Note distinction between  $V$  and V, as well as between  $W$  and W, confusing when hand-written. Also energy  $E$  and electric field  $\vec{E}$ .

# Ohm's Law

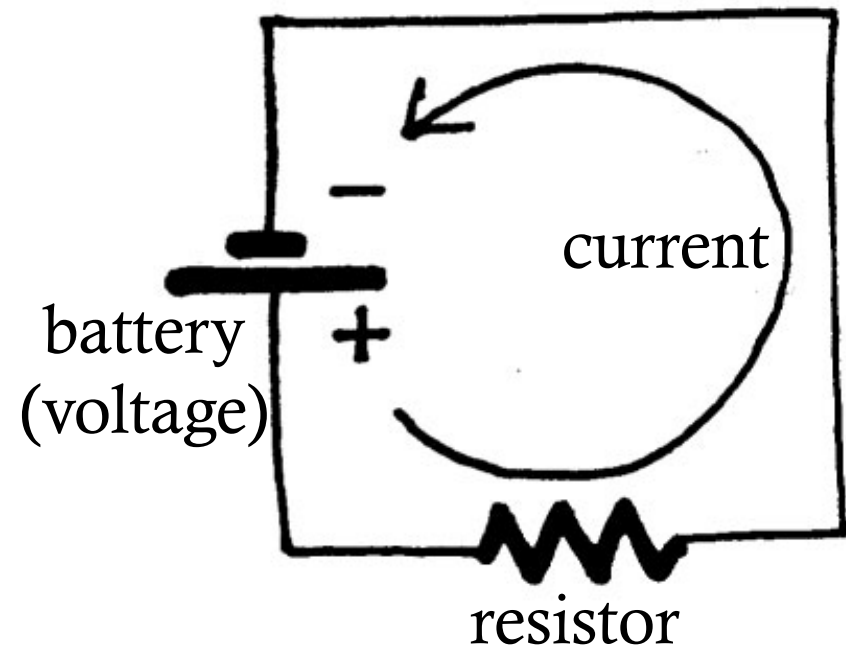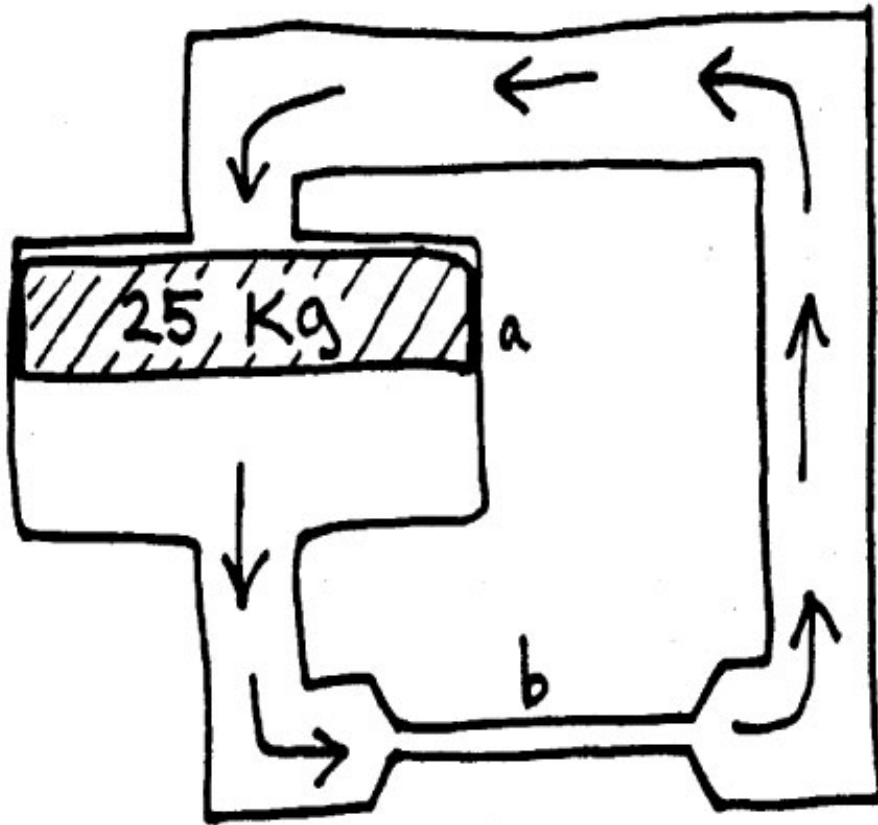

- Any good plumber understands it intuitively.
- Pressure source *a* “pushes” water through skinny pipe *b*.
- Note completed circle or “circuit”, with fat pipe (wire).
- Charge does not build up anywhere.


# Causality?

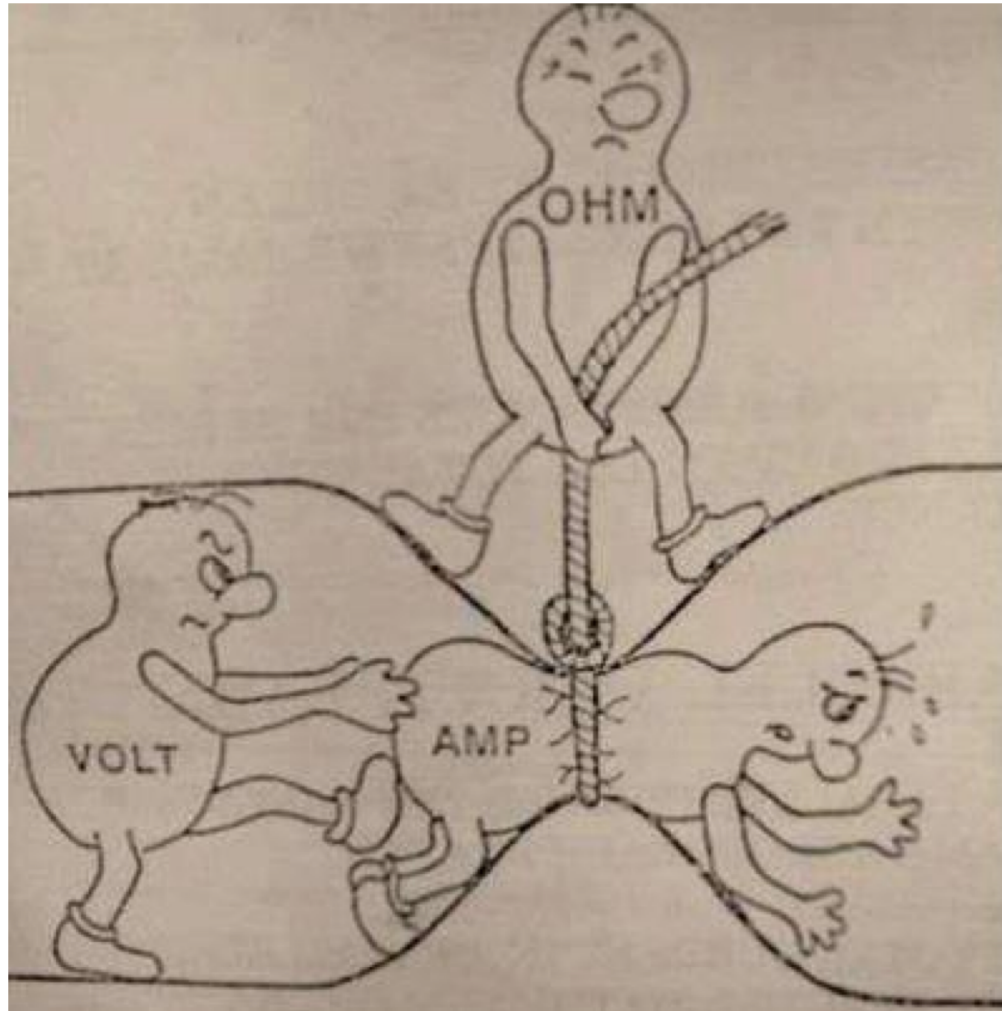

Pressure “causing” flow is a human construct...  
Current also “causes” pressure drop across resistor.



# Ohm's Law

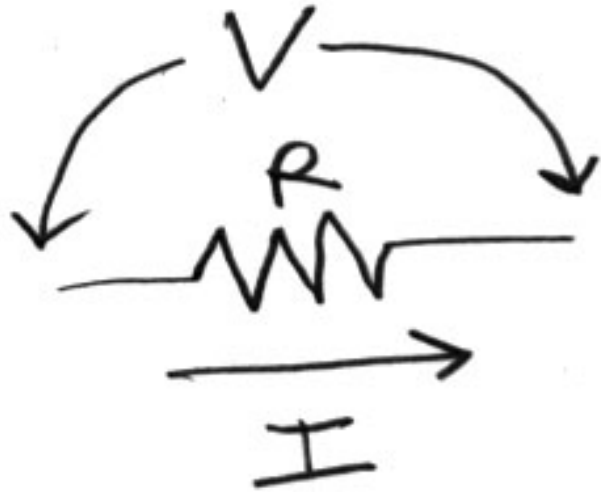

voltage *across* resistor  
current *through* resistor

$$I = \frac{V}{R} \quad \leftarrow$$


more intuitive, given a voltage and a resistance, you get a current.

$$V = IR \quad \leftarrow$$

also true; “forcing” a certain current through the resistor “generates” a voltage drop.
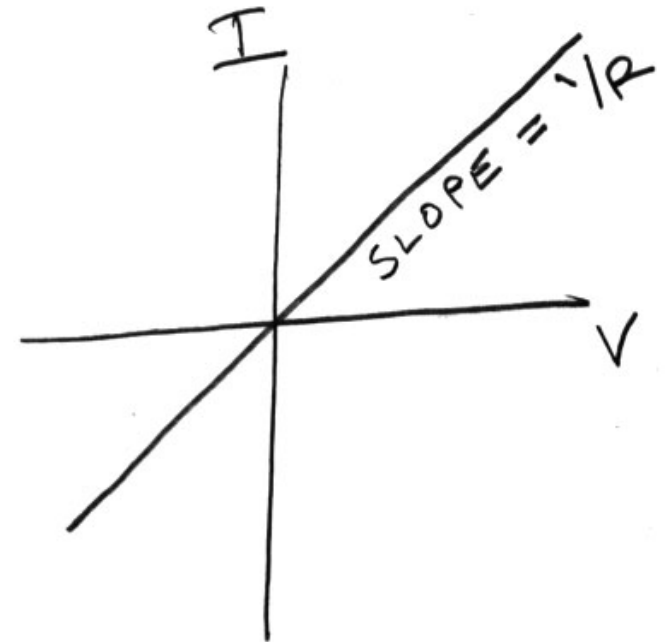
# Resistance

- Ohm's law is only an approximation, and only for components called *resistors*, but for them, linearity can be a *very* good approximation.



<u>Physical Quantity</u>	<u>Unit</u>
“ $R$ ” resistance	$\Omega$ ohm
“ $G$ ” conductance	$\Omega^{-1}$ mho

$$1\Omega \text{ (ohm)} = 1\text{V} / 1\text{A}$$

$$V = IR$$

$$1\Omega^{-1} \text{ (mho)} = 1\text{A} / 1\text{V}$$

$$I = VG$$

Note the symmetry between voltage and current 14

# Resistor Color Code

1st Digit	2nd Digit	3rd Digit
0	0	x1
1	1	x10
2	2	x100
3	3	x10 <sup>3</sup>
4	4	x10 <sup>4</sup>
5	5	x10 <sup>5</sup>
6	6	x10 <sup>6</sup>
7	7	x10 <sup>7</sup>
8	8	x10 <sup>8</sup>
9	9	x10 <sup>9</sup>

4th Band - Tolerance

10% Silver	1% 1%	0.5% 0.5%
5% Gold	2% 2%	0.25% 0.25%



1K $\Omega$  10%

Typical range:  
10  $\Omega$  – 10 M $\Omega$

<http://www.ealnet.com/m-eal/resistor/resistor.htm>

Wattage of resistor (1/4 watt, 1/2 watt) specifies guaranteed maximum continuous power before failure.

# Series Resistance $R_S$

- Same *current* through both resistors.
- Voltage across each resistor is proportional to its *resistance*.


$$V_1 = IR_1$$

$$V_2 = IR_2$$

- Total series voltage  $V_S$  is

$$V_S = V_1 + V_2$$

$$R_S = R_1 + R_2$$

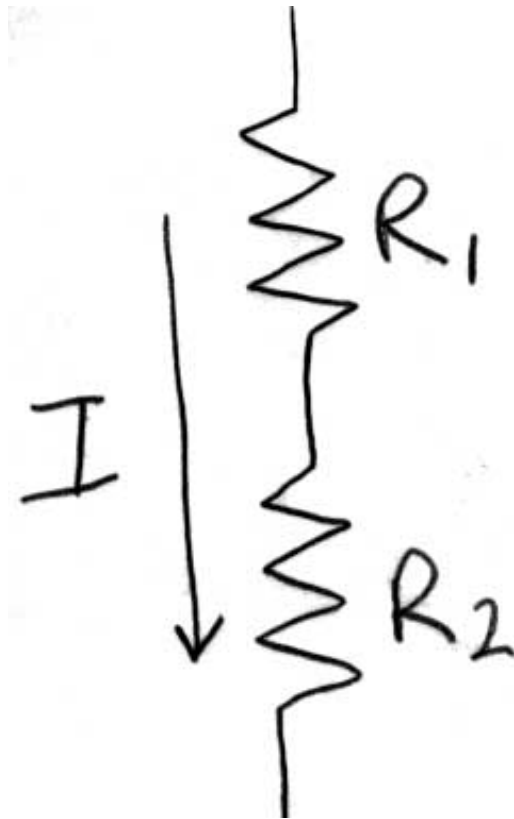

# Parallel Resistance $R_P$

- Same *voltage* across both resistors.
- Current through each resistor is proportional to its *conductance* ( $G$ ).


$$I_1 = VG_1$$

$$I_2 = VG_2$$

- Total series current  $I_S$  is

$$I_P = I_1 + I_2$$

$$G_P = G_1 + G_2$$

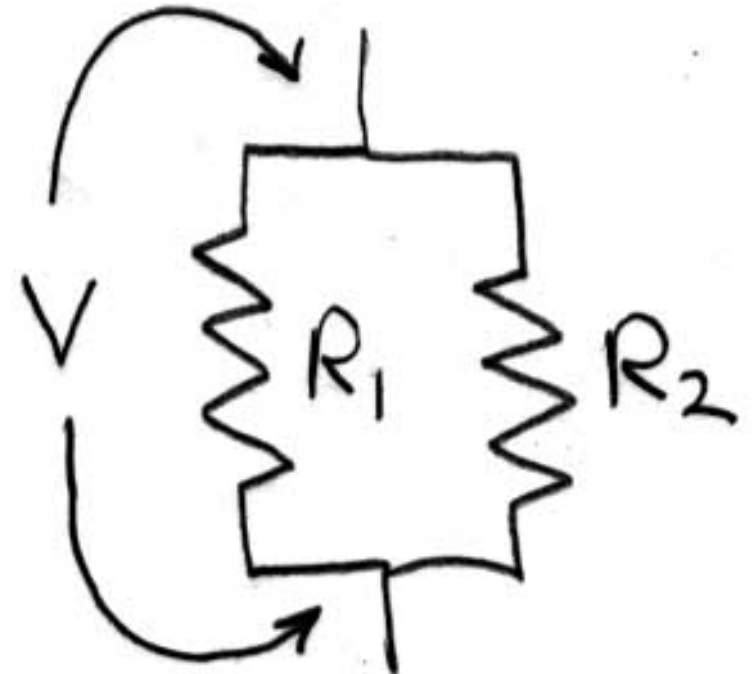

# Parallel Resistance $R_P$


- Reciprocal of the sum of the reciprocals.

$$G_P = G_1 + G_2$$

$$R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

...often rewritten as the product over the sums.

$$R_P = \frac{R_1 R_2}{R_1 + R_2}$$

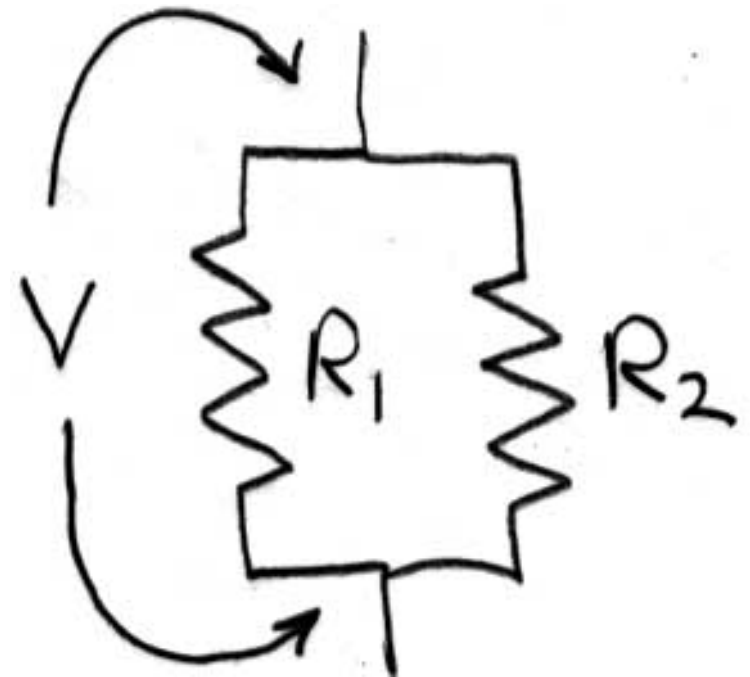


- Voltage, current, and power can be positive or negative, and the sign depends on how the voltage and current variables are defined in a given circuit.
- Power is *positive* when electrical energy is deposited in a component (resistor, light bulb, see **a**), but *negative* when energy is produced by it (battery discharging, see **b**).

$I$  is defined by convention as flowing from + to - voltage


$$P = V \times I$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

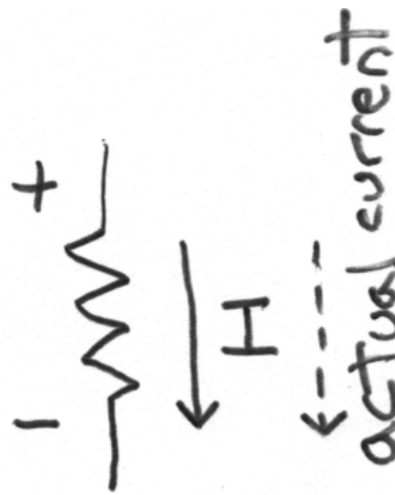

**a**

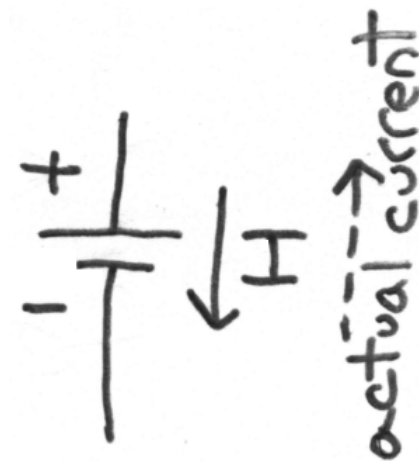


**b**

- Resistance is almost always positive, and is often considered constant, though not always (e.g. sensors such as photoresistors and thermistors).
- Voltage, current, and power can be positive or negative, constant or vary as functions of time:  $V(t)$ ,  $I(t)$ ,  $P(t)$ .
- We will first study DC (“direct current” ) circuits, where current, voltage, and power are assumed to be constant.
- DC circuits can generally be represented by fully-constrained simultaneous linear equations.


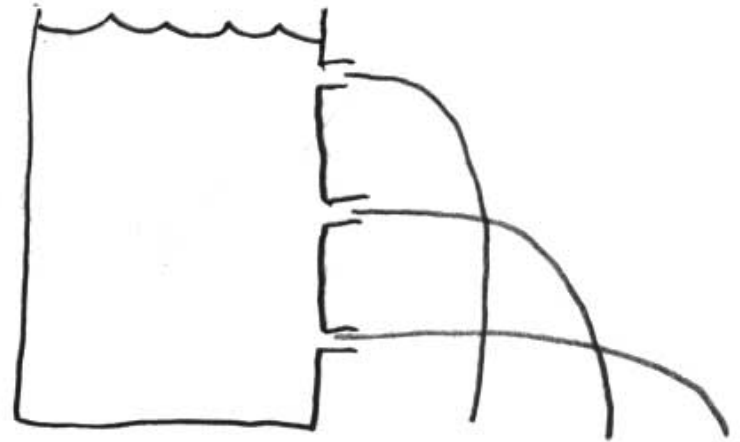
# Bad Water Analogies

- Typical bad analogy →
- Electrons rarely jump from wires. They are confined to “steel pipes” (the wires) and must return to the power source to avoid an local charge build-up or deficit.




Water shoots further from the bottom hole of the tank because pressure is greater. Not analogous to electrons, which generally do not leave the wires.
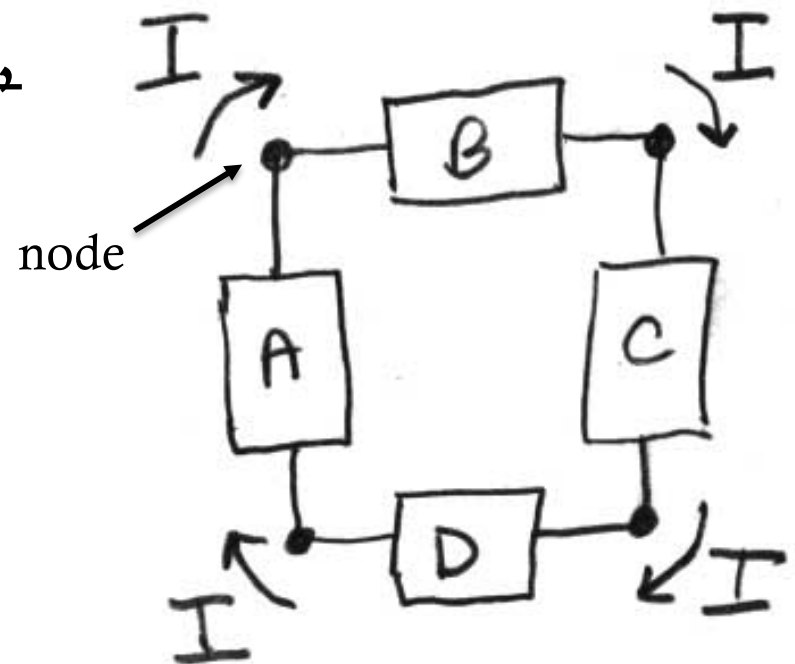
# Kirchoff's Current Law


- Charge is virtually non-compressible.
- “Components” (A,B,C,D) connect at “nodes”.
- Current around an *isolated* loop always completes the path, with  $I$  the same at every node, and local charge remaining near zero.
- At any node in any circuit,  
total current *in* equals  
total current *out*.

$$\sum_{node} I_{in} = \sum_{node} I_{out}$$


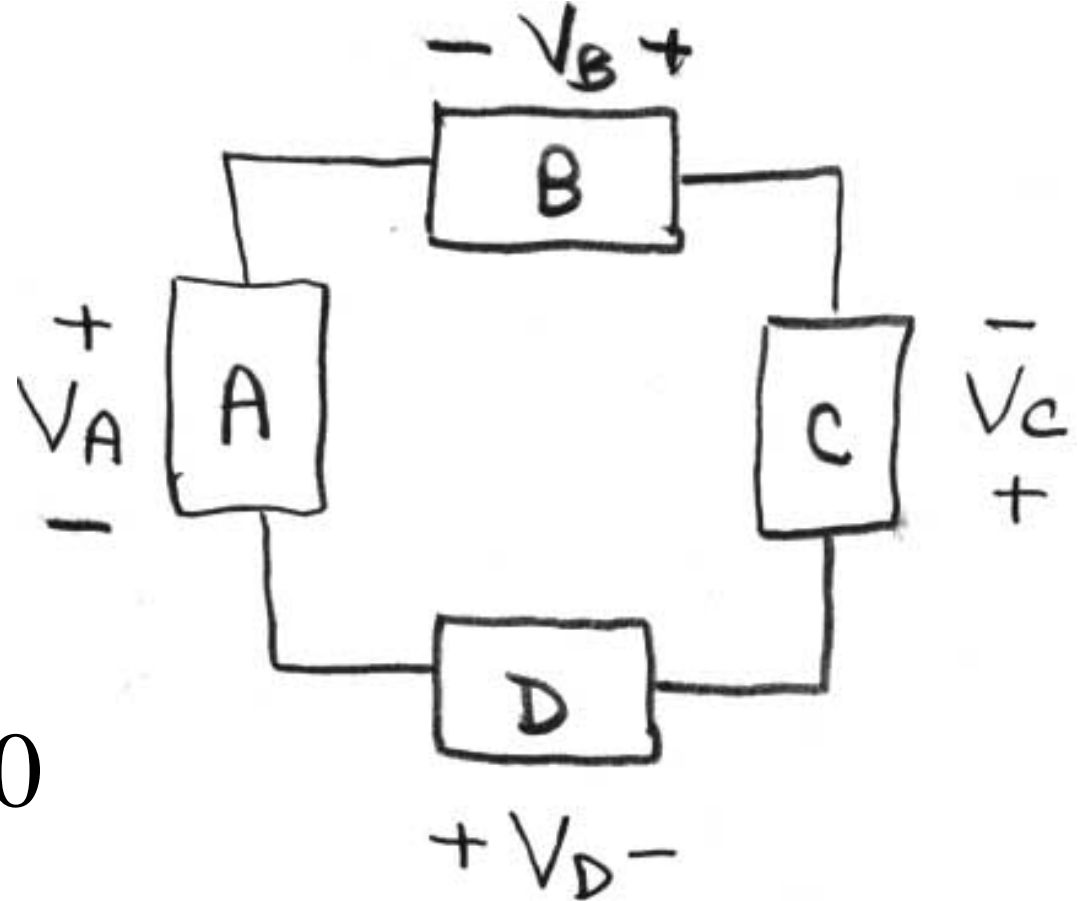
# Kirchhoff's Voltage Law

- Voltages (like pressures) add. Around any loop (not just any isolated loop) the sum of the voltages must be zero.
- The voltage relative to circuit ground must end up where it started (the same at the same node).




$$V_A + V_B + V_C + V_D = 0$$

# Kirchhoff's Voltage Law (redrawn)

- Typical schematic layout:
  - high-to-low voltage: top-to-bottom
- In this configuration Kirchhoff's Voltage Law reads:


$$V_A = V_B + V_C + V_D$$

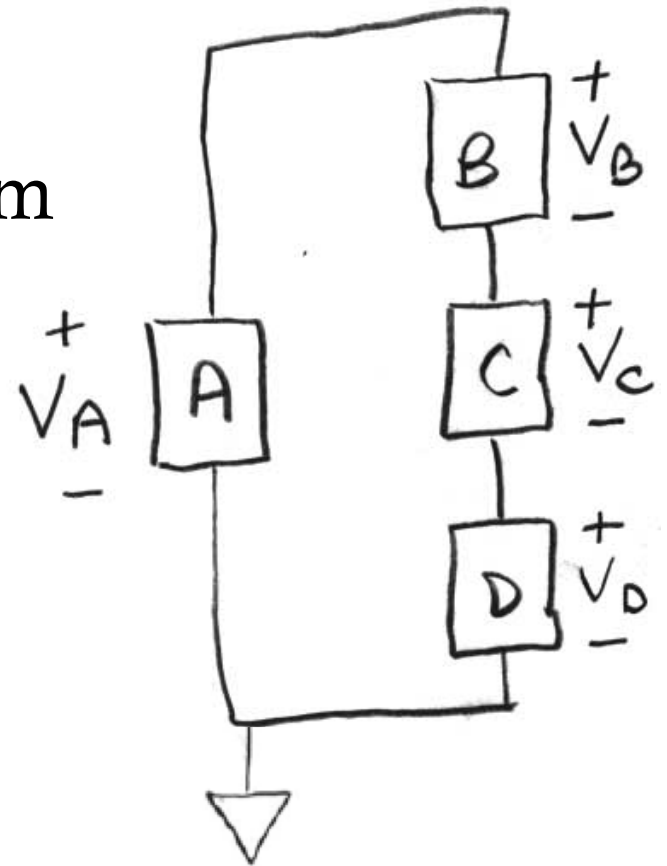

- Same voltage anywhere along any wire ( $V=IR$  and  $R=0$ ), hence the concept of node.
- Same voltage between top wire and bottom wire (ground).



Which node is  $V_C + V_D$  above ground?  $V_A - V_B$ ?
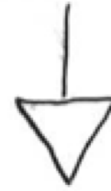
# Circuit Ground



- Defined as 0 volts, with other points in the circuit measured relative to it (voltage is always actually a difference).
- With a single-sided (not  $\pm$ ) power supply, usually the negative (black) power lead. Caution! Black=hot in house wiring, the electrician's revenge.
- Scherz differentiates analog  from digital  to keep *digital* noise away from sensitive *analog* circuits.

# Chassis Ground



- Metal box used for shielding from electromagnetic noise.
- Often the same as circuit ground.
- Beware of getting shocked if metal chassis is not also connected to “earth ground” (next slide).  
For this reason, most modern equipment has a plastic housing, especially if not using a 3-wire power cord with an earth ground.

# Earth Ground



- Copper pipe struck into the ground.
- One of the few cases where the non-compressibility of electrons does not apply; You can pour large numbers of electrons into the earth without raising its voltage, as pouring water into the ocean does not raise the sea level.
- Earth ground is important to consider for safety, since when touching a circuit with one's finger, one's feet on the floor can complete a dangerous circuit that includes the heart.


# Safety - Electrocution

- 110 volts AC can kill (>500 deaths/year in US)
- Skin resistance  $\sim 1\text{M}\Omega \gg$  internal resistance of tissue; minimum at 60 Hz (“impedance” can vary with frequency, as we shall see).
- Water, especially with salt (sweat; ocean) reduces skin resistance (used in lie detectors).
- Usually by inducing arrhythmia. Keep current away from heart.
  - Electricians wear dry shoes with rubber soles and keep 1 hand in pocket.
  - Birds sitting on one power line don't get shocked.
- Can cause tetanus; you can't let go and neither can the person who grabs you to pull you away.


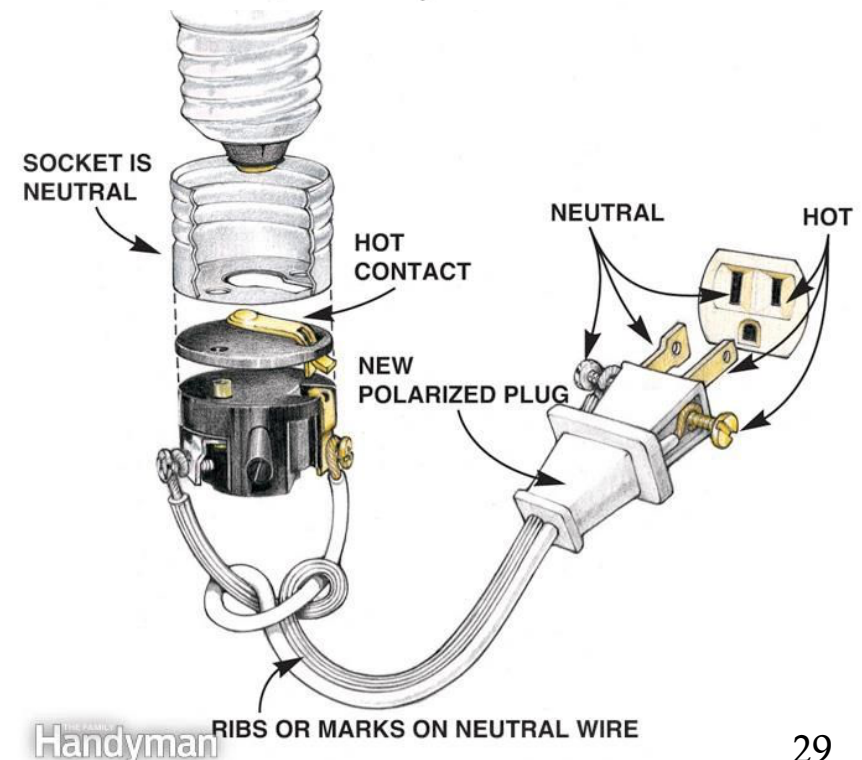
# Safety – Wall Socket


- Current comes “out”\* *hot* lead (small rectangular hole) and “returns” through *common* (or “neutral”) lead (large rectangular hole).
- Size difference prevents 2-lead devices like lamps from being plugged in backwards, which would make the outer part of the lamp socket hot.
- *Earth ground* (round hole) connects to pipe in the ground where power enters the house.



\* alternating current (AC) actually goes both ways.

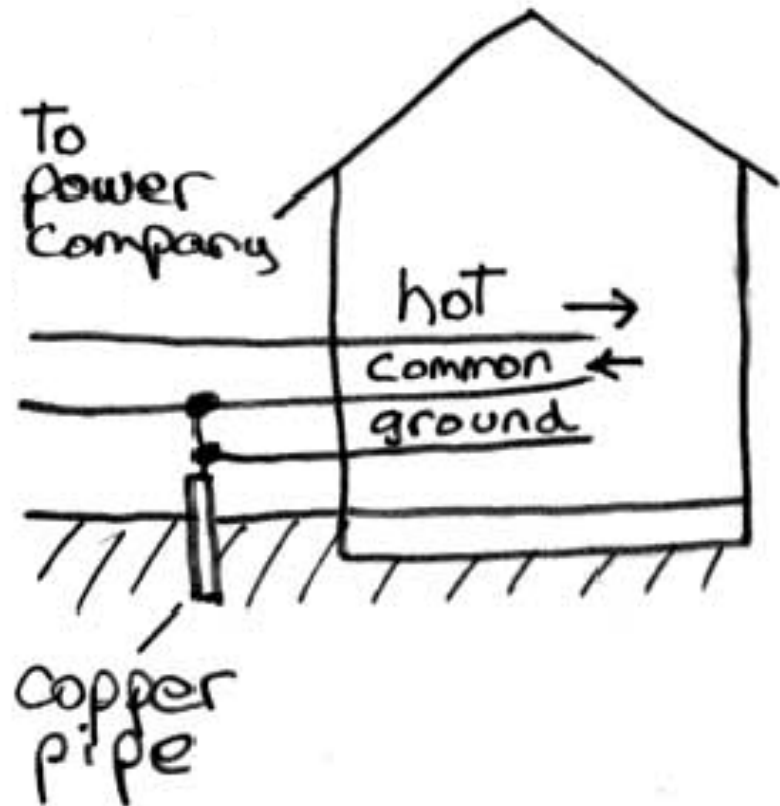
# Safety – Wall Socket

- Ground Fault Interrupter (GFI) in kitchen and bathroom disables power if current out *hot* lead does not match current returning in *common* lead (may be going through human to ground instead).
- To the electrician, black is *hot*, to electrical engineer it is *circuit ground*.


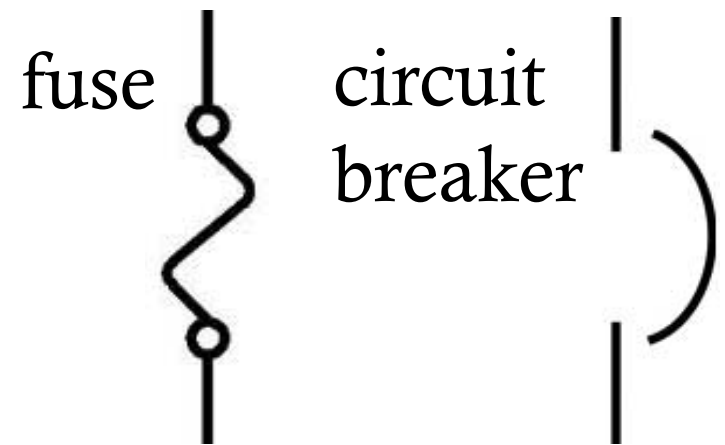
# Safety – Fire

- Even low power can heat things up over time especially with an unlimited power source (wall socket); Energy is integral of power over time.
- Temperature equilibrates with dissipation of heat through conductivity, convection, and radiation.
- Heat is generated where there is resistance to the current in a circuit,  $P = I^2R$  (bad contact in wall socket or extension cord for space heater).
- *Fuses* (low melting metal with higher resistance) and *circuit-breakers* (thermal or magnetic) form weak link, typically limiting 120V circuits to 15A or 30A.



# Safety – Static/Lightening

- Static due to friction and dry conditions generally safe to humans; although very high voltage (50,000 V/inch), current is very low.
- Static can destroy integrated circuits (ICs), especially with field-effect (high impedance) transistors. ICs come in conductive packages and personnel wear grounded wrist-straps.
- Lightening (and static) is plasma and does not obey Ohm's law. Generally safe inside a car.

# Safety – Lab

- Solder contains lead. Do not eat it. The smoke from soldering comes primarily from “flux”, a resin core in the solder that cleans the surfaces being soldered.
- Turn off the soldering irons at the end of the lab. If you drop one, don’t grab for it.
- Clipping wires can send fragments flying. Be careful of your own and other’s eyes.
- Don’t use large power supplies in the lab, as they can damage the MicroBLIP, computers, and can make components smoke.



# Ideal Voltage and Current Sources

- Ideal voltage source holds *voltage* constant no matter what. Voltage placed across resistor “causes” current...

$$I = \frac{V}{R}$$


- Ideal current source holds *current* constant no matter what. Current forced through resistor “causes” voltage...

$$V = IR$$

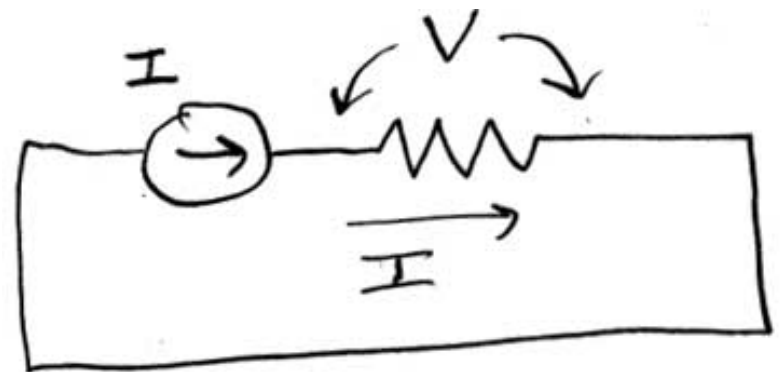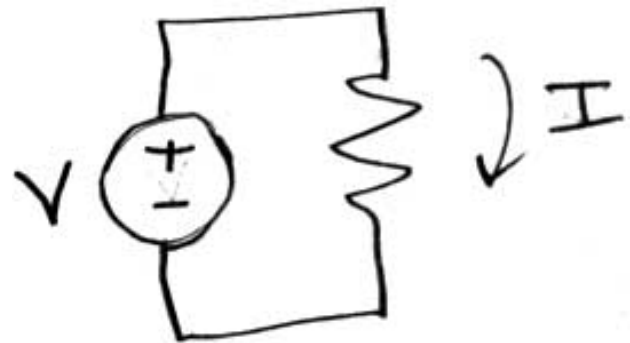


What is resistance (“output impedance”) of ideal voltage and current sources?

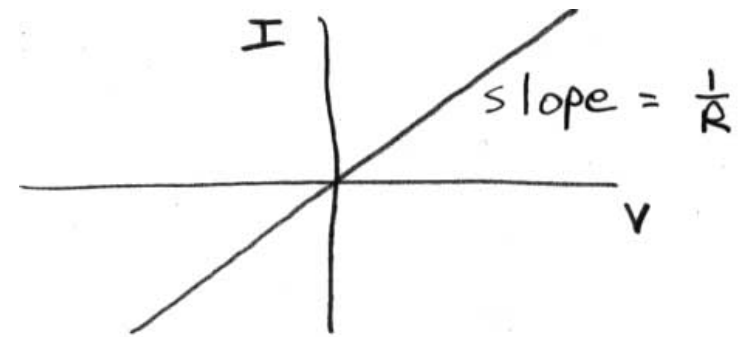
Recall for a resistor it is  $1/\text{slope}$  on plot of  $I$  vs.  $V$ .



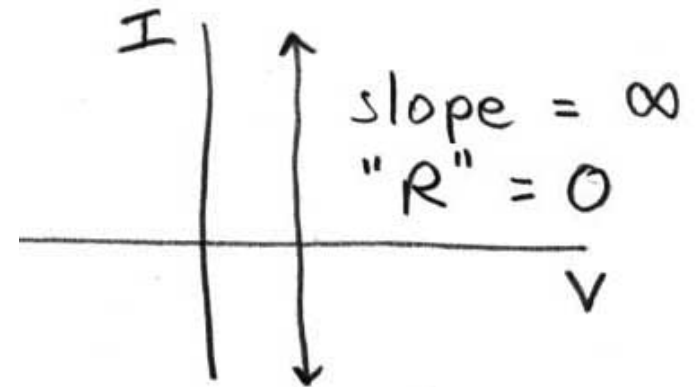Ideal *voltage* source has zero output impedance.



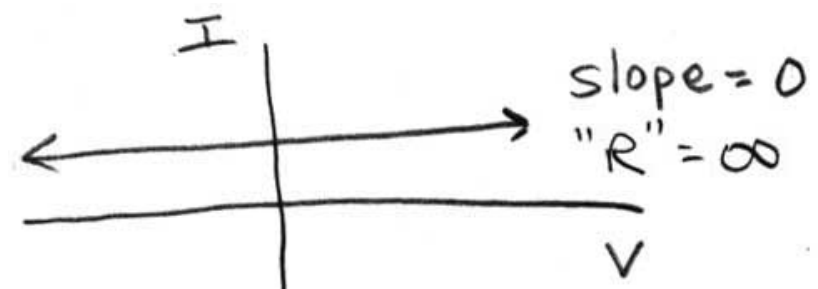Ideal *current* source has infinite output impedance.




# Voltage Divider

- View as “system” with voltage input and output.
- Same *current* through both resistors (assuming no current going to the output).
- Therefore, voltage across each resistor is proportional to its *resistance*.

$$I = \frac{V_{\text{in}}}{R_1 + R_2} \quad \begin{array}{l} \text{resistance} \\ \text{adds in} \\ \text{series} \end{array}$$

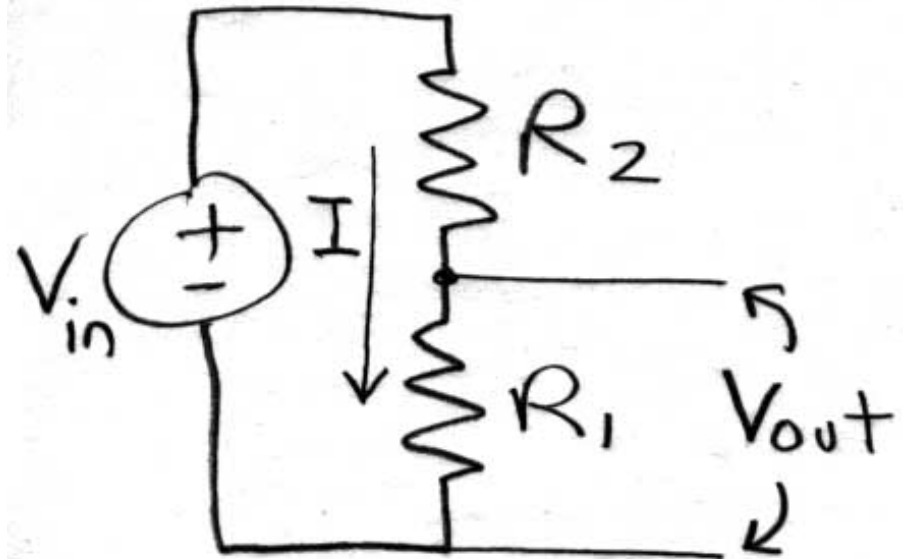
$$V_{\text{out}} = IR_1 = \frac{R_1}{R_1 + R_2} V_{\text{in}}$$





# Example

10 V

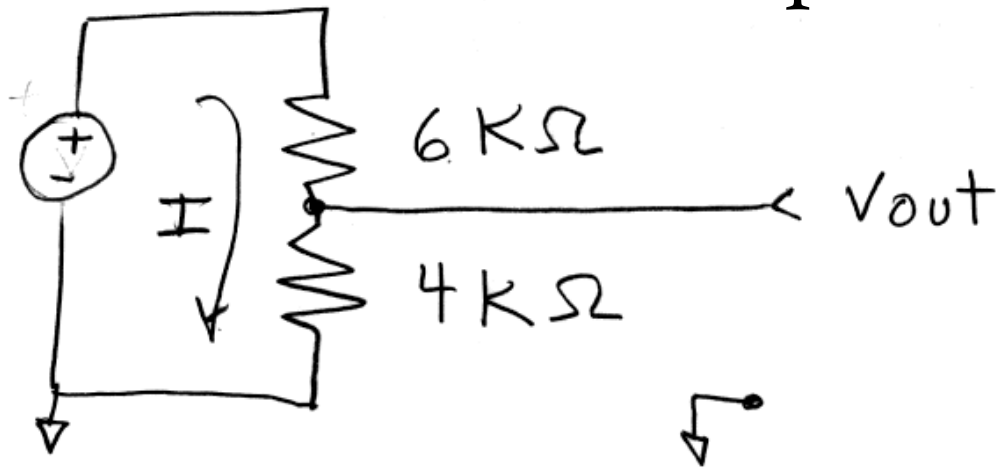

Voltage  
"Divider"

Same I through both resistors  
total resistance  $10\text{ k}\Omega$

$$I = \frac{10\text{ V}}{10\text{ k}\Omega} = 1\text{ mA}$$


$$V_{\text{out}} = 1\text{ mA} \cdot 4\text{ k}\Omega = 4\text{ V}$$

leaves 6V across top resistor

Voltage across each resistor proportional to its resistance.
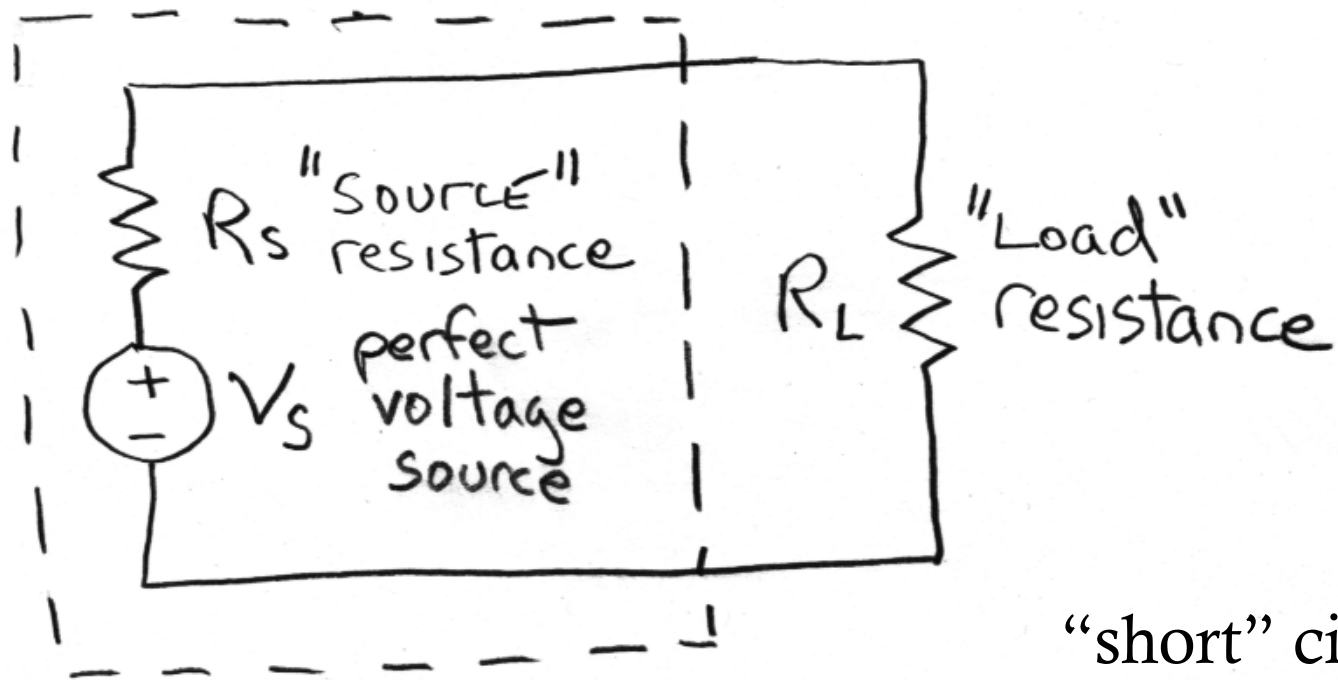
# Real Voltage Source

$$R_{\text{Source}} \ll R_{\text{Load}}$$



"short" circuit




- Limits maximum current to  $\frac{V_S}{R_S}$  when  $R_L = 0 \Omega$
- Car batteries have low  $R_S$  to deliver high currents.

# Current Divider

- View as “system” with current input and output.
- Same *voltage* across both resistors.
- Current through each resistor is proportional to its *conductance*.


$$I_{\text{in}} = V(G_1 + G_2) \quad \begin{array}{l} \text{conductance} \\ \text{adds in} \\ \text{parallel} \end{array}$$
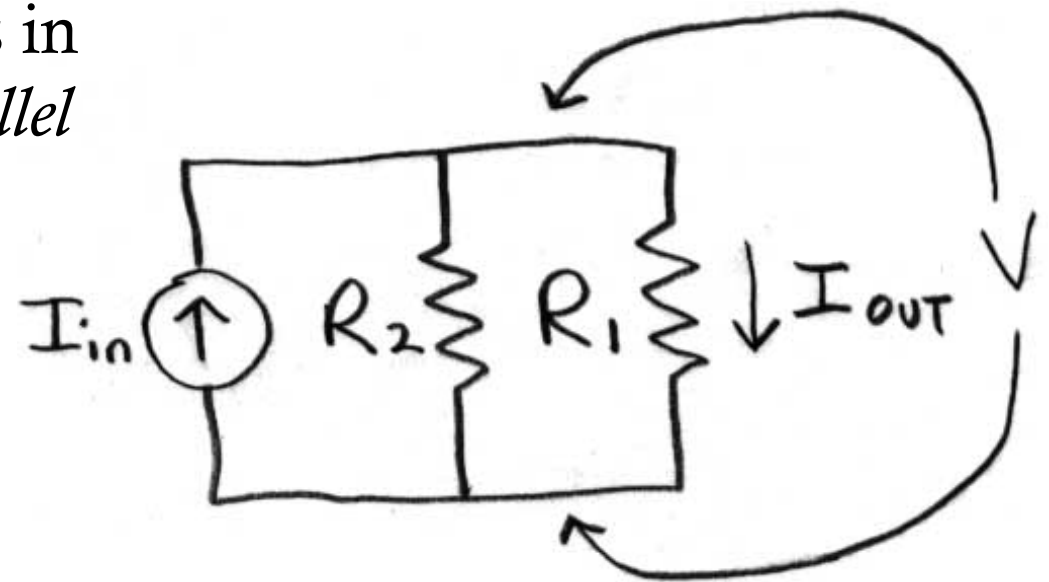
$$I_{\text{out}} = VG_1 = \frac{R_2}{R_1 + R_2} I_{\text{in}}$$


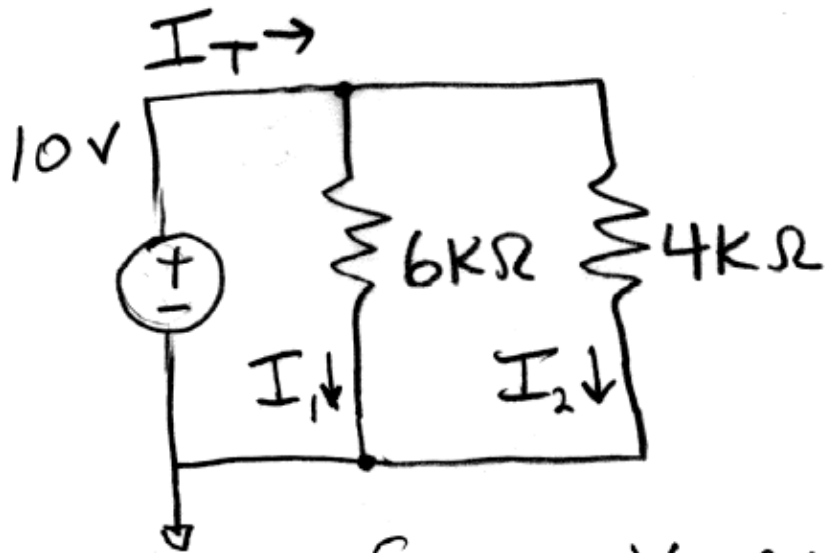
# Example

(should move this slide to after 37 next year)



Parallel Resistors

Same V across both resistors


$$I_1 = 10V / 6k\Omega = 1.66 \text{ ma}$$

$$I_2 = 10V / 4k\Omega = \underline{2.5 \text{ ma}}$$

$$I_T = 4.16$$
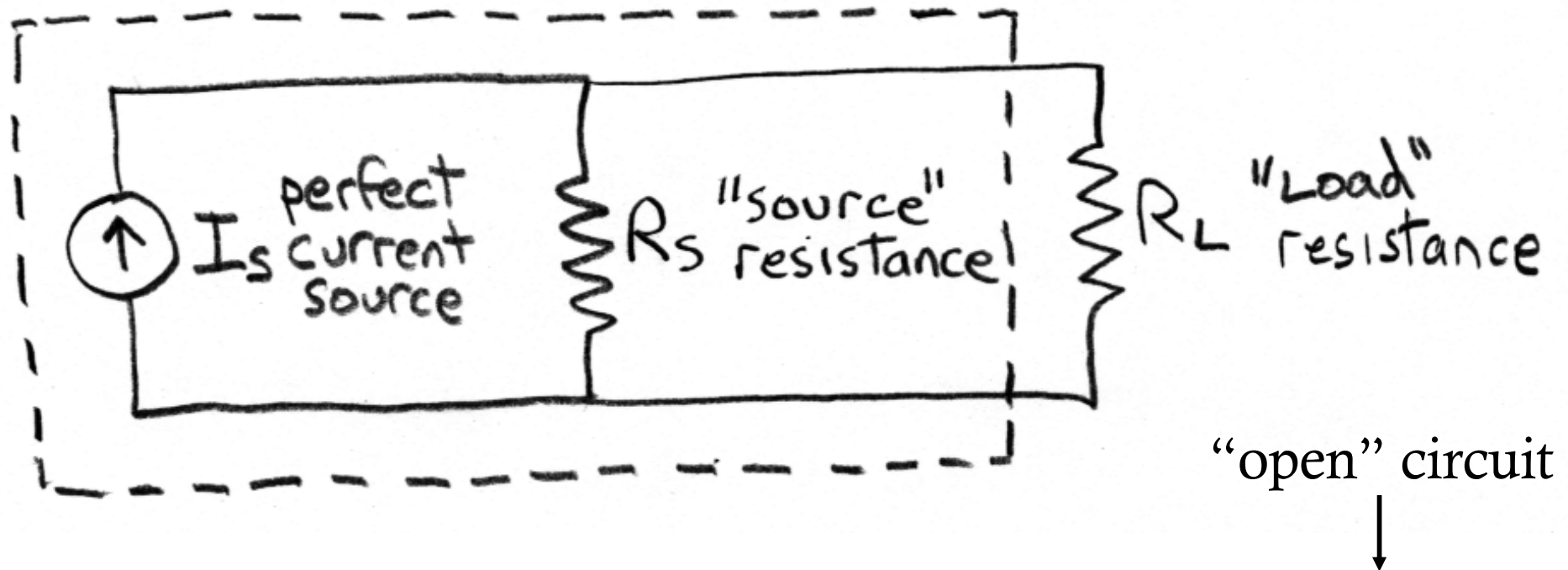
# Real Current Source

$$R_{\text{Source}} \gg R_{\text{Load}}$$




- Limits maximum voltage to  $I_s R_s$  when  $R_L = \infty \Omega$
- Static electricity has high  $R_s$  to deliver high voltages (at low currents).
- Why do we need ideal current and voltage sources? (as offsets in the linear equations for DC circuits)
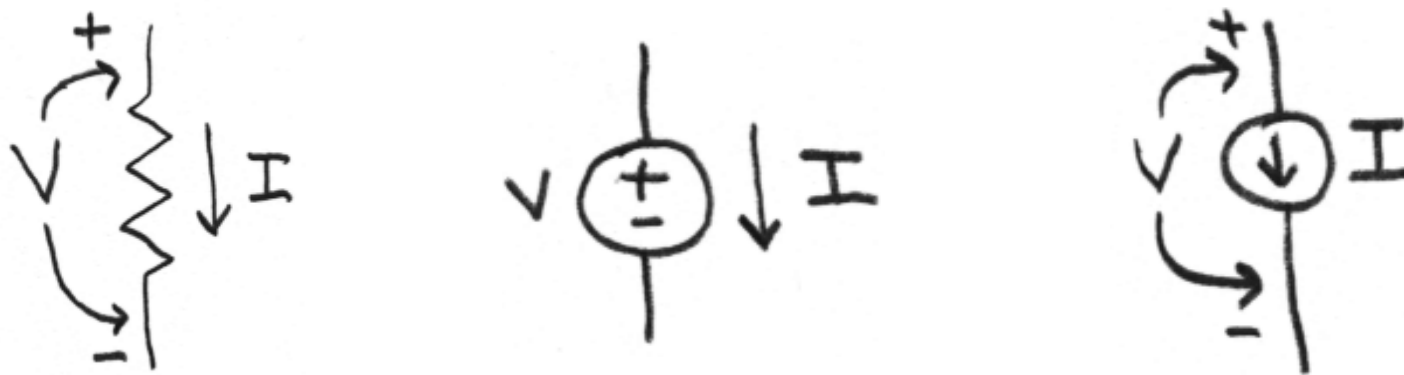
# More about positive and negative power.

- The voltage across any component and the current through it are always defined as being in the same “direction,” with the current running through the component from + to – voltage.

directions voltage and current variables defined by convention




- In a resistor, this always leads to positive power (power delivered *to* the component, making it warm). They are passive devices obeying Ohm’s law (recall the current vs. voltage graph).
- Voltage and current sources normally show negative power (power delivered *from* the component), but only when *they* are the cause of resulting current or voltage. When a battery is charged by an external source, it exhibits *positive* power.

# Example: positive and negative power.

- Voltage and current sources can be forced to produce positive power, as in this circuit where the current source is “charging” a battery (voltage source), forcing current to flow into the battery “against” the voltage.

$$P = 2V \times 2A \\ = +4W$$

$$P = (-2V) \times 2A \\ = -4W$$

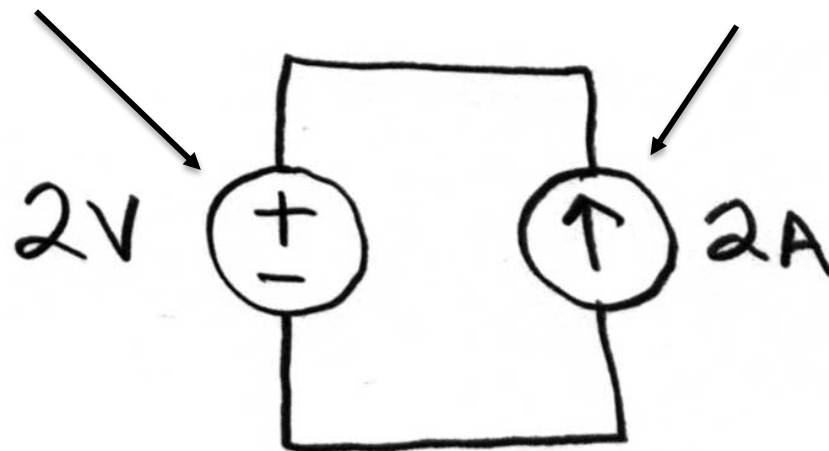


- The current source is delivering power to the voltage source.
- Total power for the circuit is zero (energy is conserved).
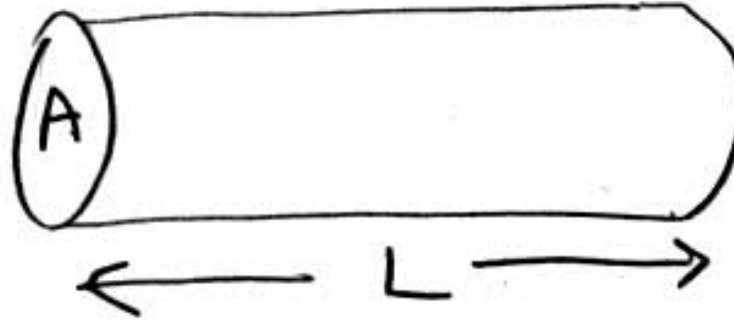
# Resistivity of materials

- A resistor consists of a material with a shape.

assume a cylinder  
length  $L$ , area  $A$



$$R = \rho \frac{L}{A}$$

- *Resistivity*  $\rho$  in ohm-meters

insulator (glass, quartz)  $10^{16}$ - $10^{10}$   $\Omega\text{M}$

semi-conductor (silicon)  $10^3$ - $10^{-5}$   $\Omega\text{M}$

conductors (metal)  $10^{-6}$ - $10^{-8}$   $\Omega\text{M}$

superconductor 0  $\Omega\text{M}$

- *Conductivity*  $\sigma \equiv \frac{1}{\rho}$



# American Wire Gauge (AWG)

AWG number (solid)	Diameter (inches)	Resistance per 1000 ft (ohms)
20	0.0320	10
18	0.0403	6.4
16	0.0508	4.0
14	0.0640	2.5 *

\* 14-gauge has twice diameter of 20-gauge and  $\frac{1}{4}$  resistance




- Although we have been assuming wire has zero resistance, over long distances the resistance does become significant.
- The table above is for copper wire.
- Copper has a lower resistivity than silver or gold (!)
- Gold used for contacts because it doesn't corrode.
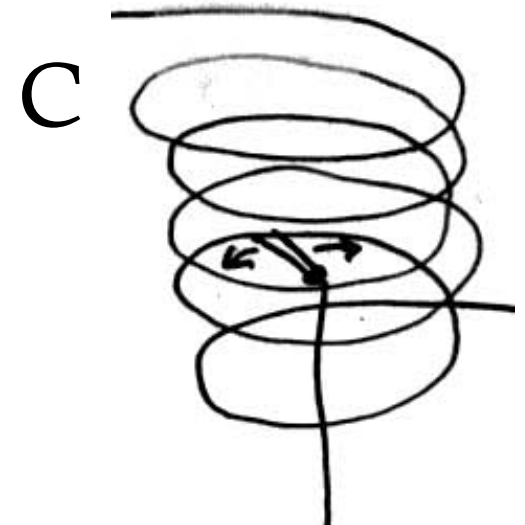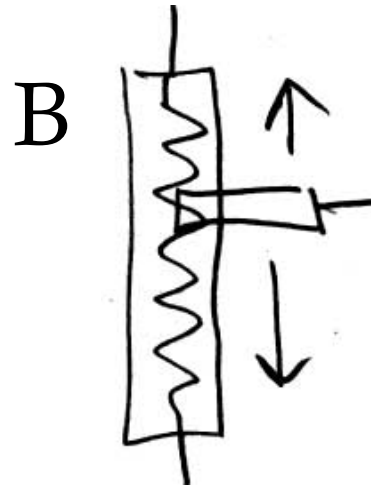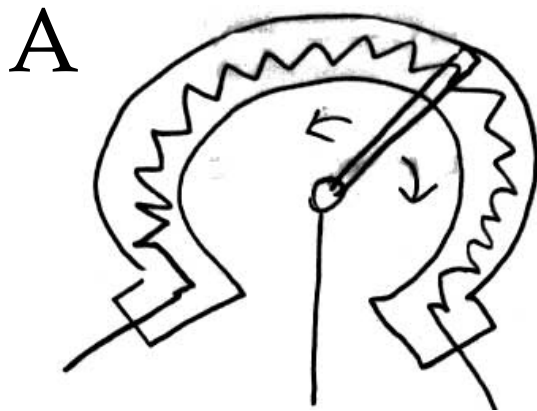
# Potentiometer – “Pot”



Three-terminal device:  
fixed resistor with a  
movable wiper.

Physically: (A) single-turn wiper on a circular resistor, (B) “linear” wiper on straight resistor, (C) multi turn wiper on spiral resistor (accurate).



Linear vs. Logarithmic (audio) taper.

# Potentiometer – “Pot”


- Ignore one lead and you have a simple two-lead variable resistor.
- Typical use: producing a variable fraction of voltage source  $V_S$ ; pot provides both resistors of a voltage divider with output between 0 and  $V_S$ .



sometimes drawn as



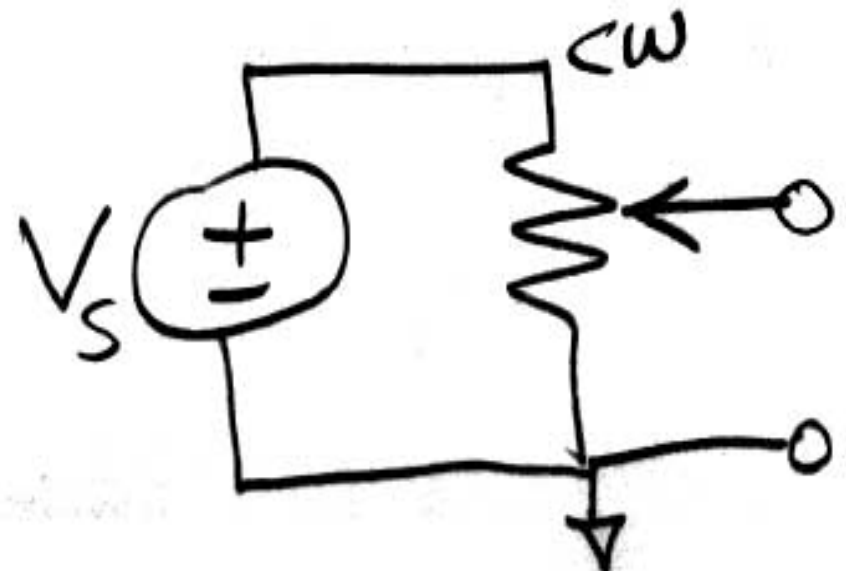“cw” wiper at this end when turned clockwise



# Real Resistors and Pots


- Resistors generally  $1\Omega$  to  $20M\Omega$
- 5% tolerance  $\frac{1}{4}$  or  $\frac{1}{2}$  watt common



ceramic for high wattage



accurate linear pot

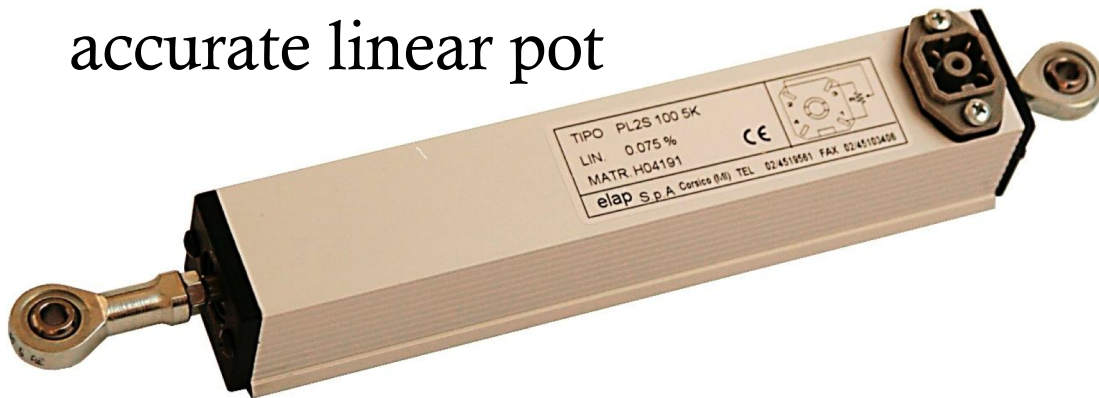

stereo log taper pot




“trim” pot




# What to Ignore...

- Estimate the total resistance:

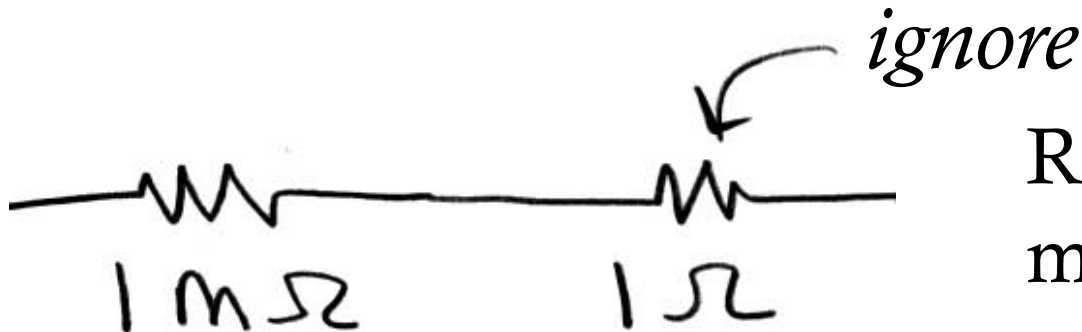

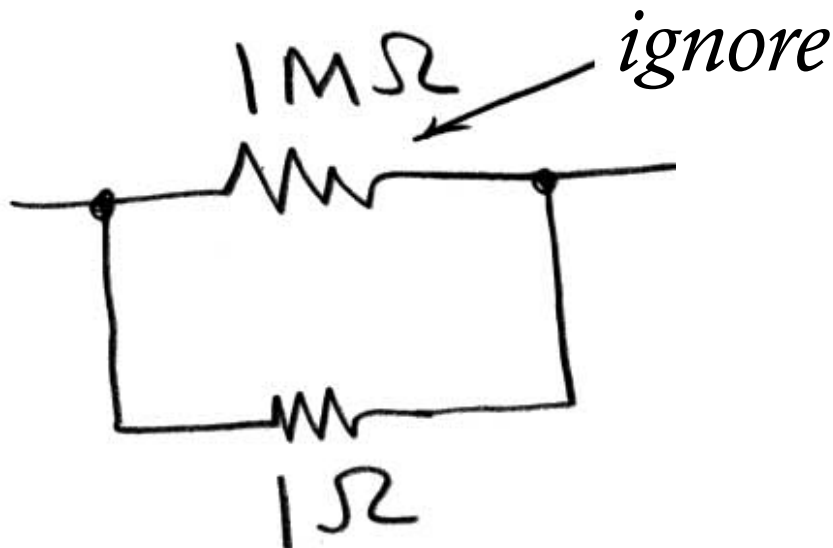Resistors in *series*:  
much smaller resistor is essentially a “short circuit” or piece of wire.  $\sim 1\text{ M}\Omega$






Resistors in *parallel*:  
much larger resistor is essentially a “open circuit” or insulator.  $\sim 1\ \Omega$

- Keep tolerance of resistors in mind (e.g. 5%).

# Simplifying resistor networks

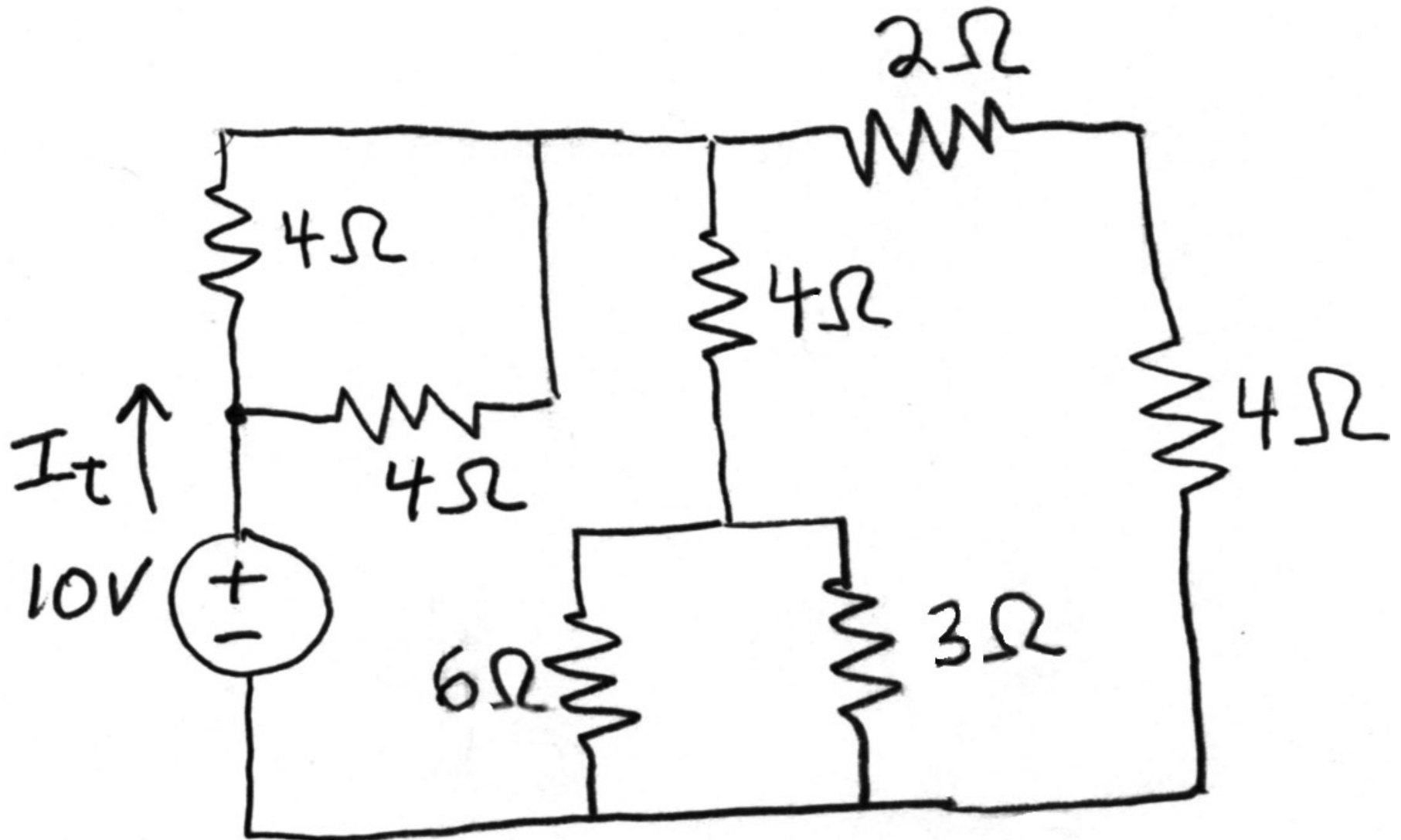
Example: compute currents through each resistor



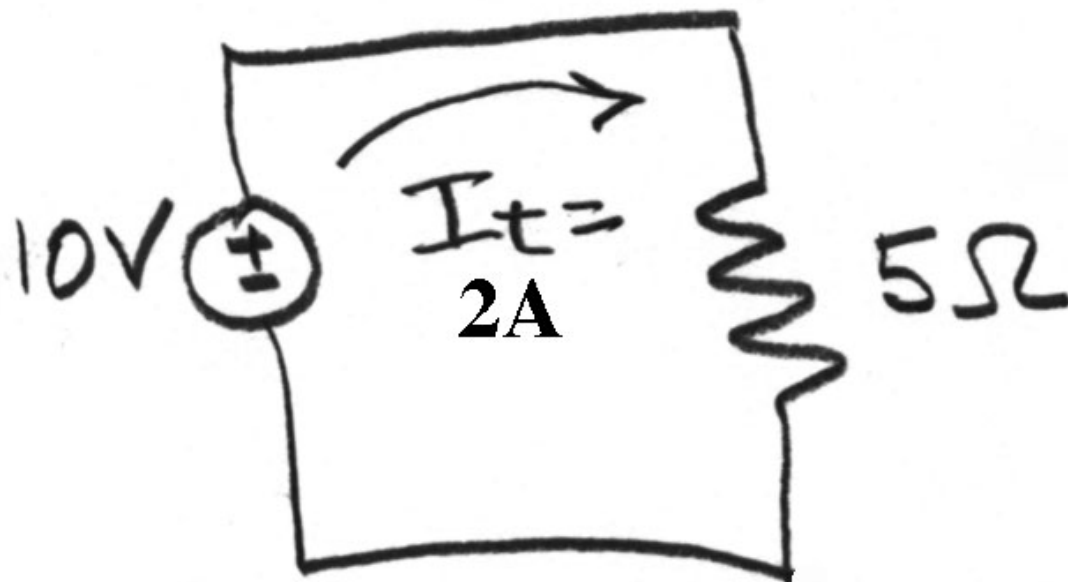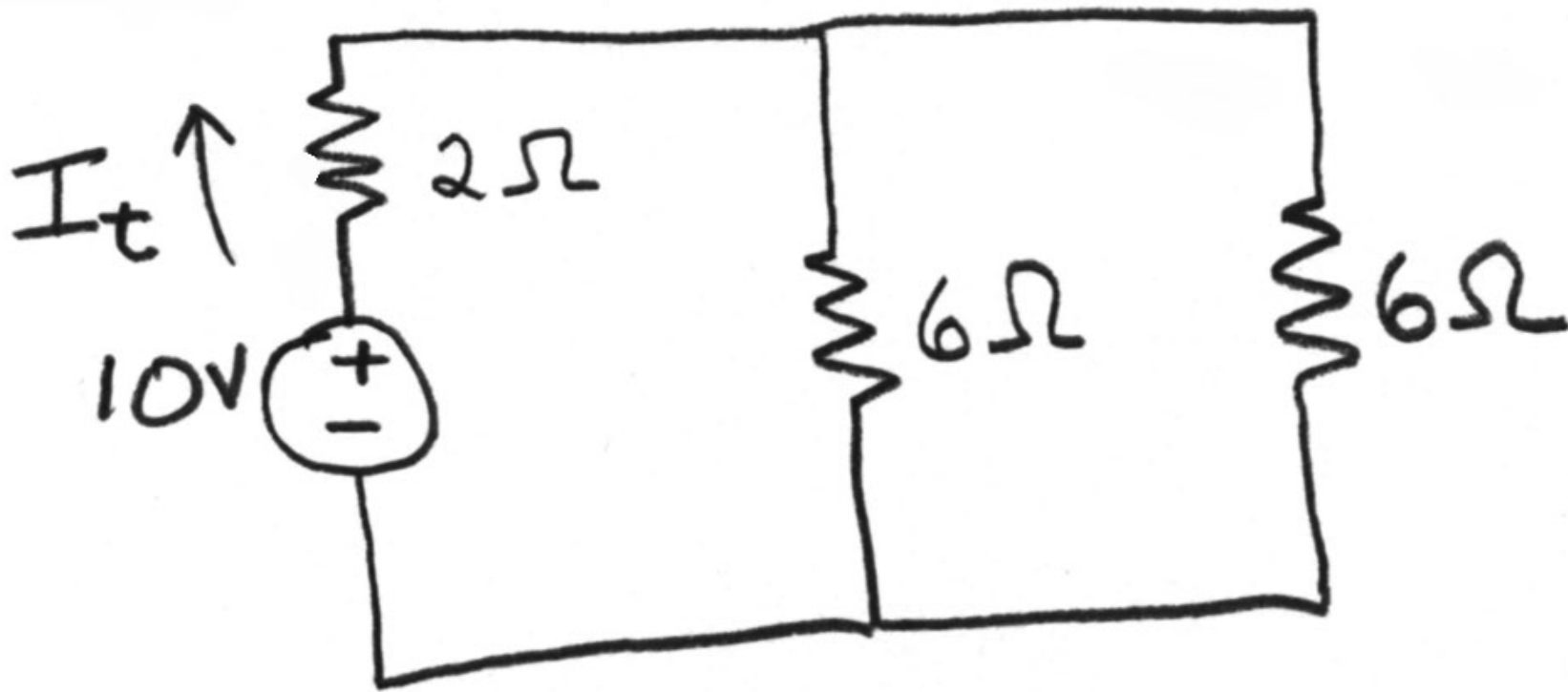

Equivalent  
simplified  
circuits

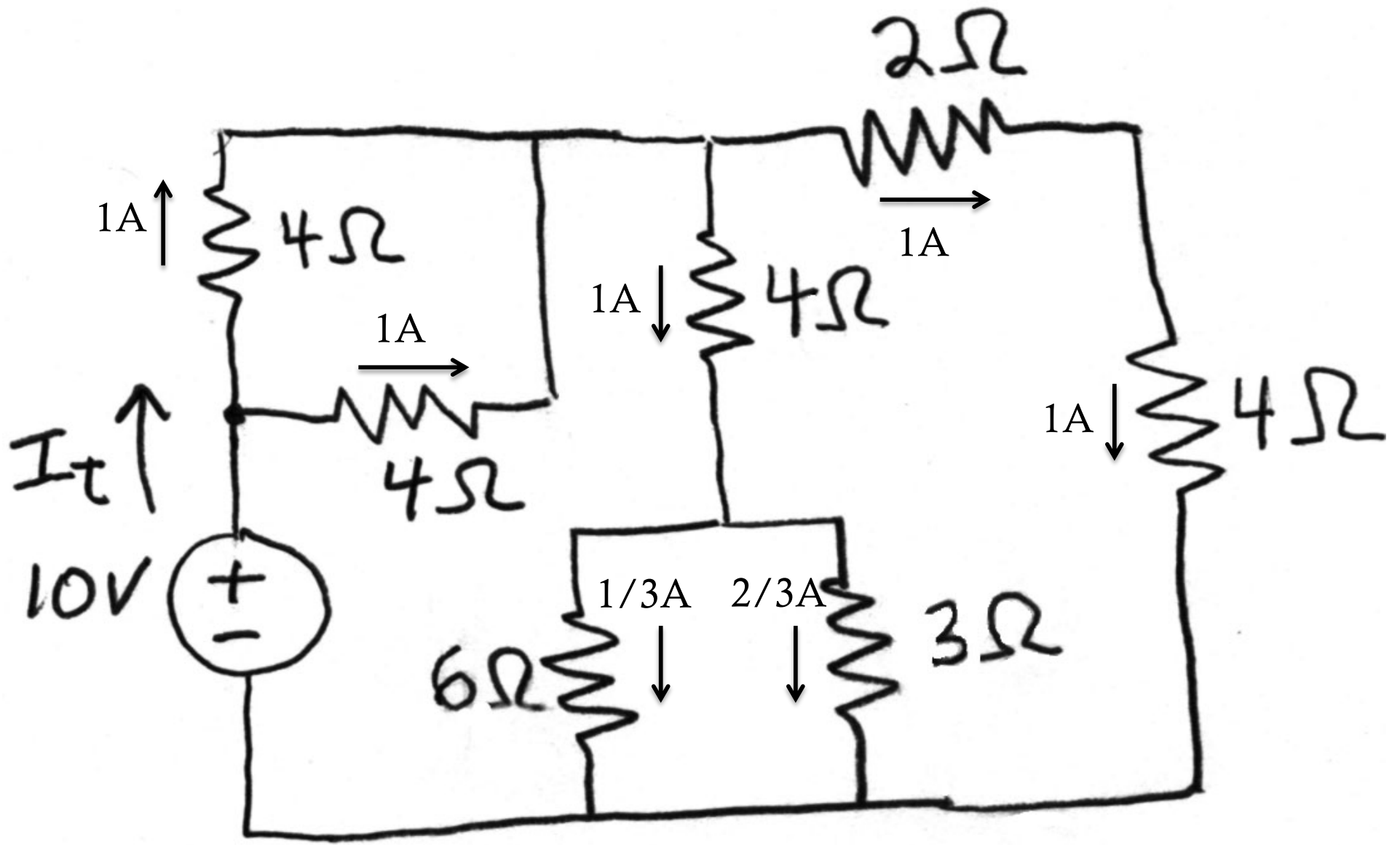With total of 2A, compute individual currents






# Thevenin Equivalent

ANY NETWORK OF




's

and

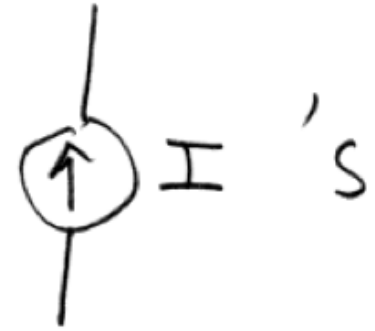

can be redrawn as

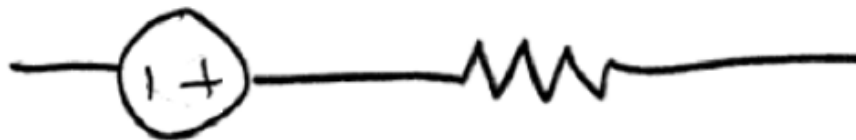


# Norton Equivalent

ANY NETWORK OF



's,

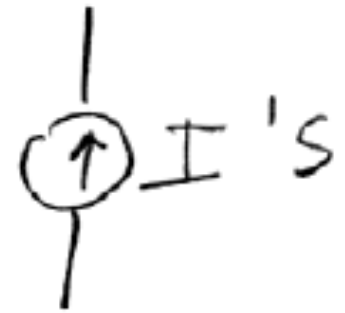


and




Can be redrawn as



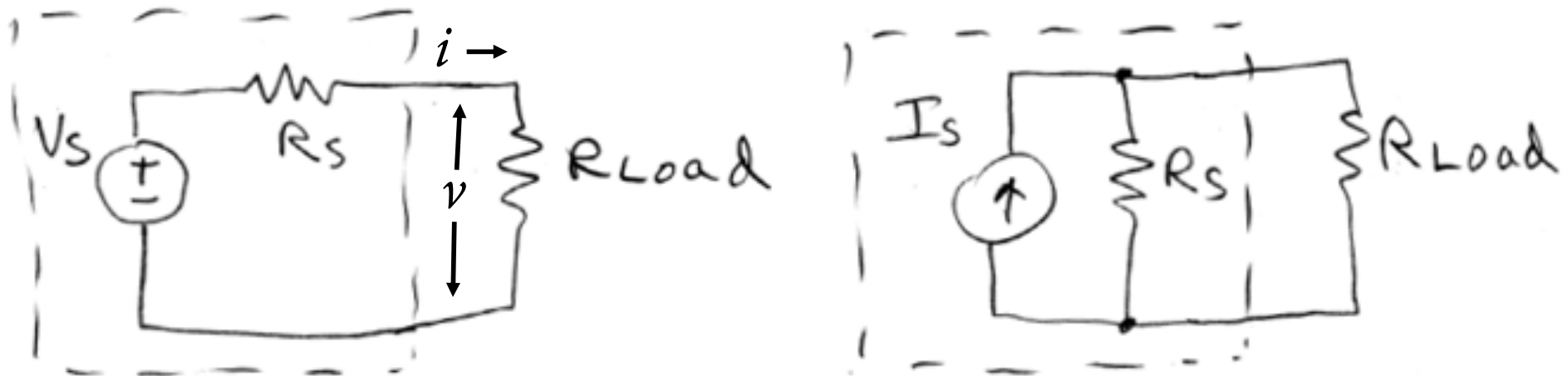These 2 sources behave the same with respect to  $R_{\text{Load}}$  if  $I_S = \frac{V_S}{R_S}$




Output (Load) Current vs. Voltage

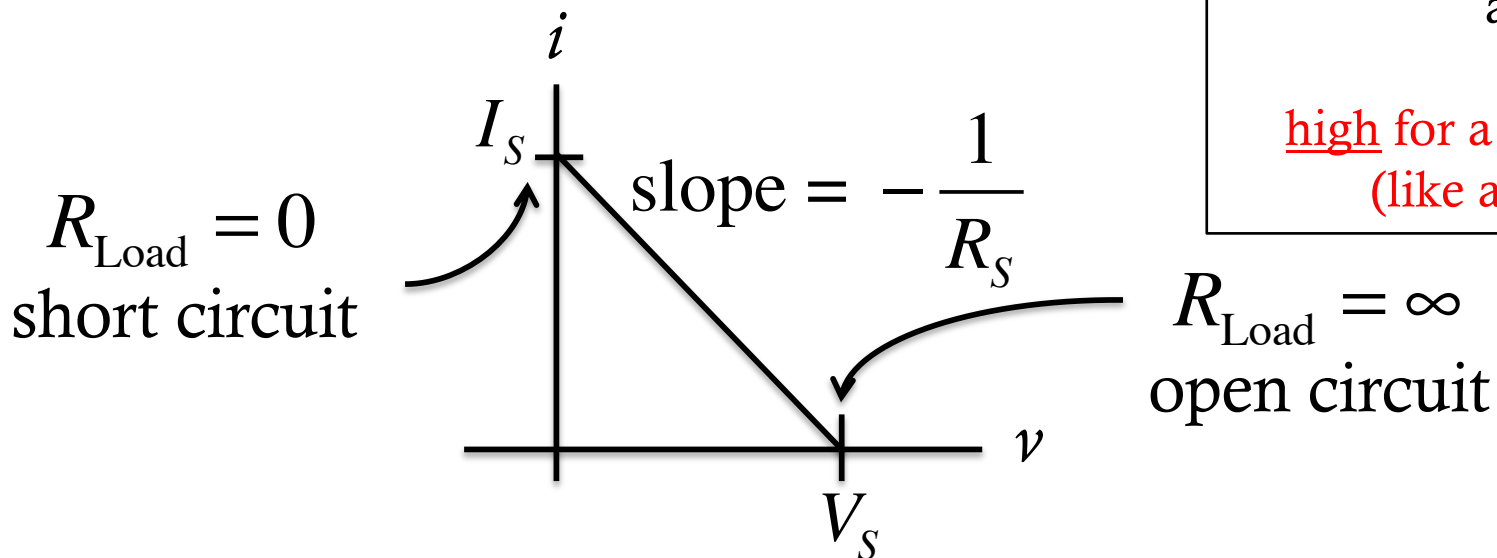


$R_S$  (source resistance) also called “output impedance” should be:  
low for a **real voltage source** (like a battery)  
**and**  
high for a **real current source** (like a leaky faucet).

These two types of sources are called “Thevenin” and “Norton”

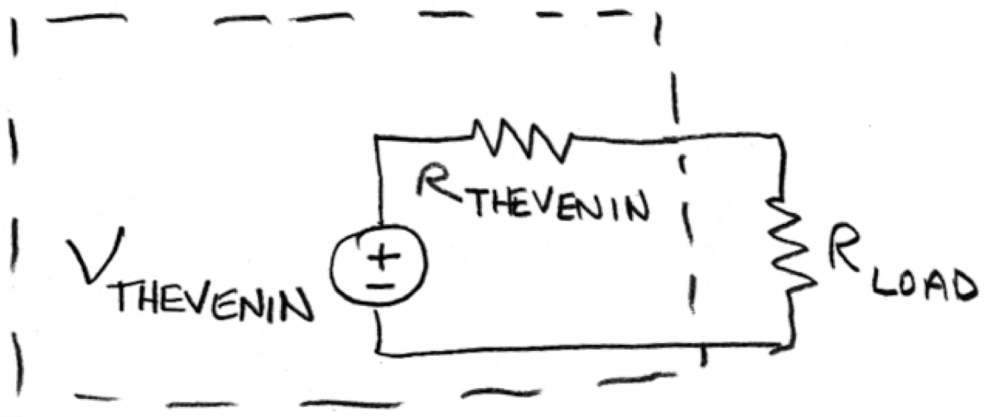Two sources behave the same with respect to  $R_{Load}$  if  $I_{Norton} = \frac{V_{Thevenin}}{R_{Thevenin}}$




*Thevenin equivalent*

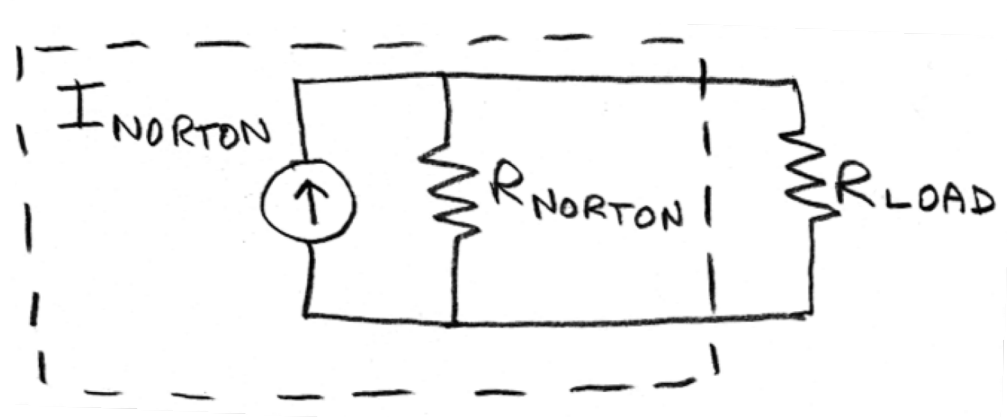

*Norton equivalent*


Output (Load) Current vs. Voltage

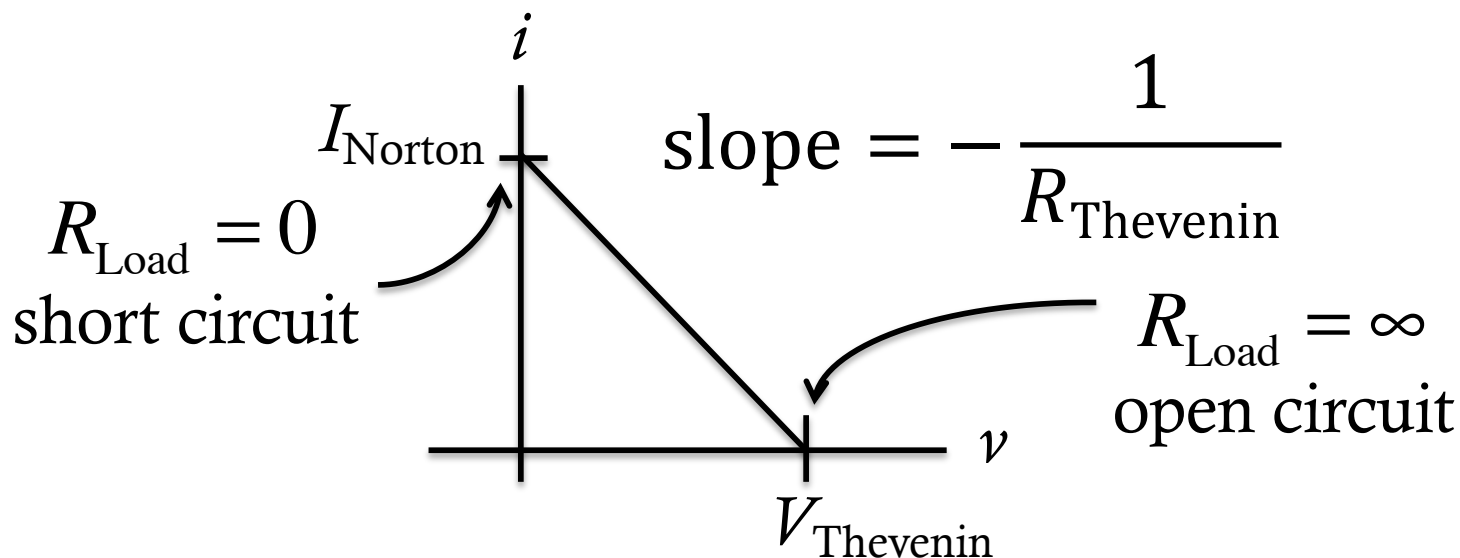

By definition:  
 $R_{Thevenin} = R_{Norton}$   
 (same as  $R_S$  on  
 previous slide)

# Thevenin Equivalent - Example

What is current through  $R_3$  ?

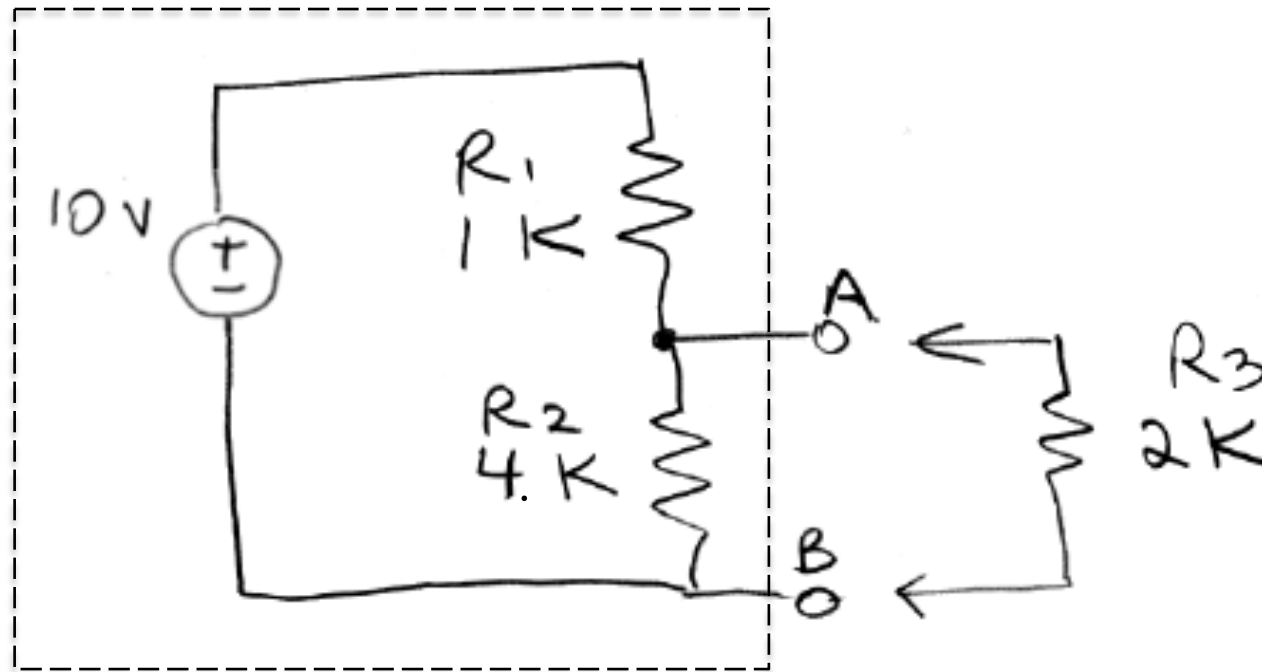


- Find  $V_{\text{THEV}}$  of “branch” (2-node component)
  - Compute voltage between A and B without  $R_3$  “open circuit”

$$V_{\text{THEV}} = 10\text{V} \frac{4\text{K}}{1\text{K} + 4\text{K}} = 8\text{V}$$

(continued...)

- Now, to find  $I_{\text{NORT}}$ 
  - Short the output, compute current through “short circuit”
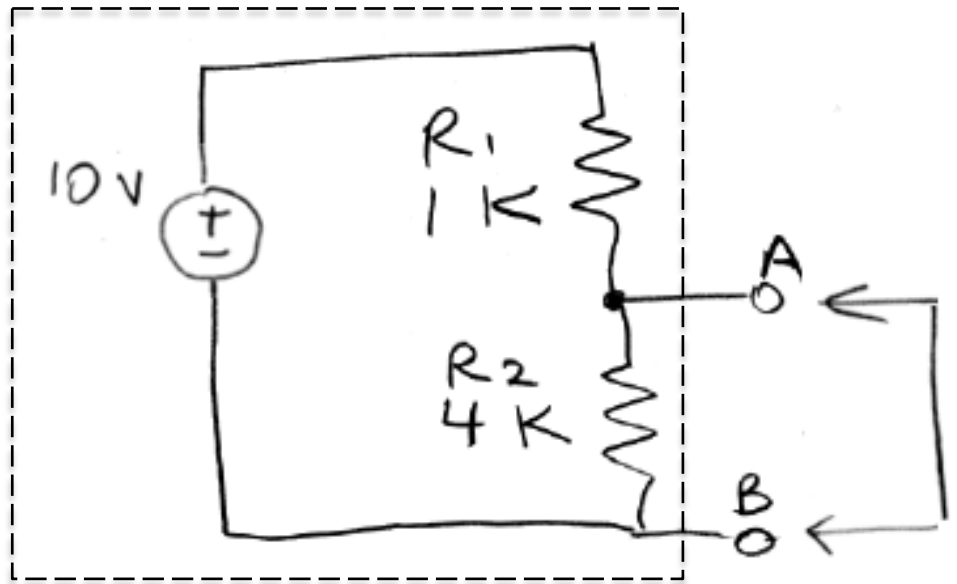
$$I_{\text{NORT}} = \frac{10\text{V}}{1\text{K}\Omega} = 10\text{mA}$$




- Use  $V_{\text{THEV}}$  to find  $R_{\text{THEV}}$  given  $I_{\text{NORT}}$ .

$$R_{\text{THEV}} = \frac{8\text{V}}{10\text{mA}} = 800\Omega$$


(continued....)

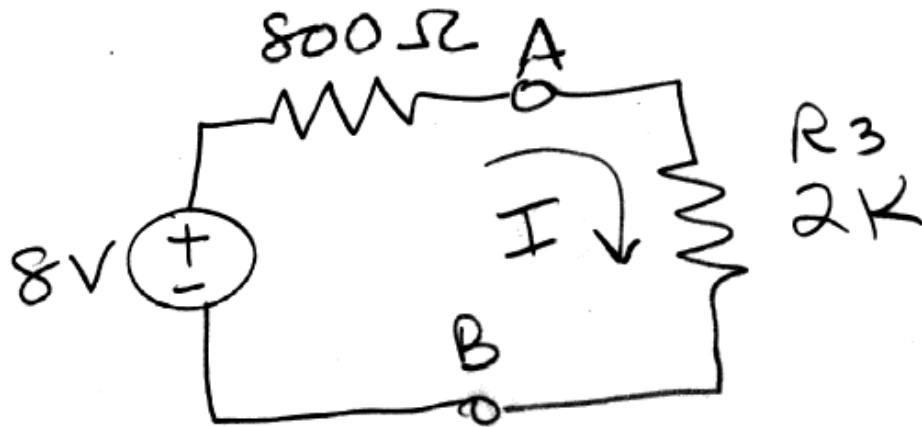- Use  $V_{\text{THEV}}$  to find  $I$  through  $R_3$ .



$$I = \frac{8V}{2K + 800\Omega} \cong 3mA$$

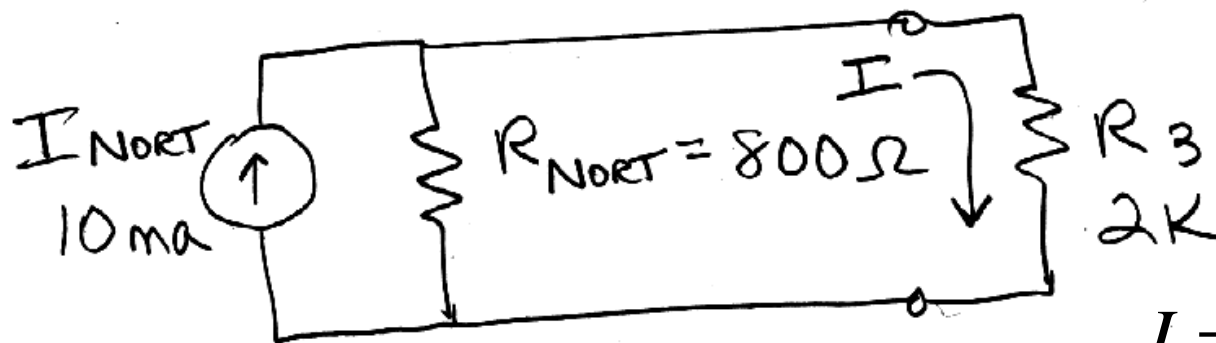- Use  $I_{\text{NORT}}$  to find  $I$  through  $R_3$ .





Use the current divider equation

$$I = I_{\text{NORT}} \frac{R_{\text{NORT}}}{R_3 + R_{\text{NORT}}} \cong 3mA$$
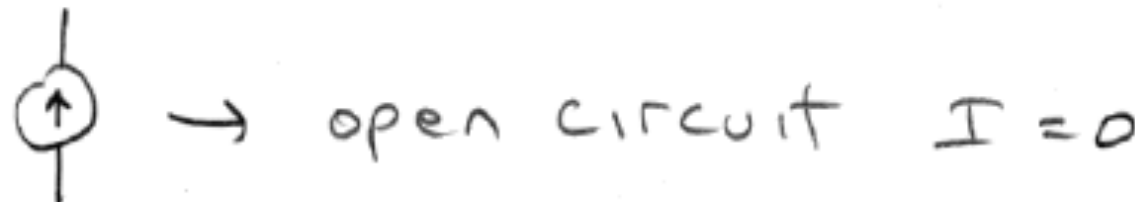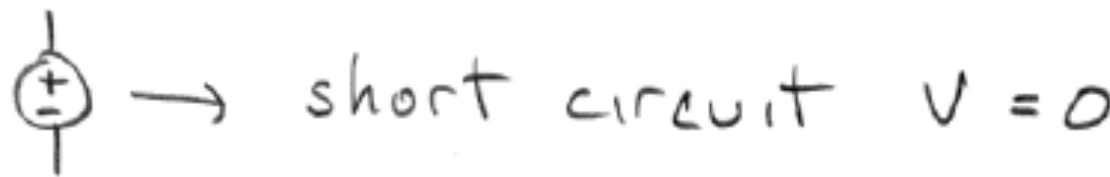
# Superposition Theorem

- The current in a branch (or voltage across) is the sum of the currents (or voltages) produced by each source individually, *with all other sources set to 0*.
- The currents through (and voltages across) each component add independently (linearly).
- Setting a voltage source to 0 V means a short circuit (piece of wire).
- Setting a current source to 0 A means an open circuit (removed).





# Superposition Theorem - Example




Solve for  $I_1$  as the sum of two currents,  $I_{11}$  and  $I_{12}$



Setting  $I_B$  to zero (open circuit)

$$I_{11} = \frac{V_A}{R_1 + R_2}$$

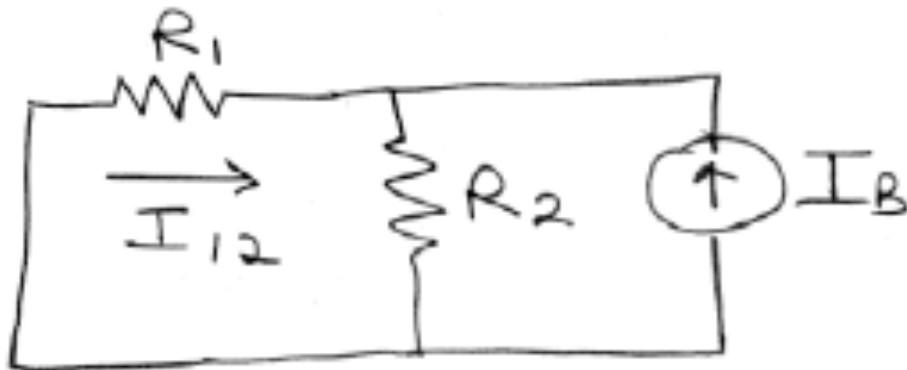

Setting  $V_A$  to zero (short circuit)


$$I_{12} = -\frac{I_B R_2}{R_1 + R_2}$$

Current divider, current going the other way.

Add the two independent currents together:

$$I_1 = I_{11} + I_{12} = \frac{V_A - I_B R_2}{R_1 + R_2}$$
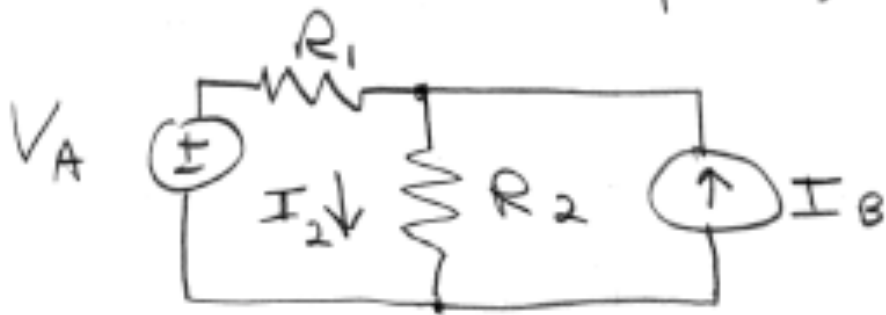
# Superposition Theorem – Example (cont.)




Solve for  $I_2$  as the sum of two currents,  $I_{21}$  and  $I_{22}$



Setting  $I_B$  to zero (open circuit)

$$I_{21} = \frac{V_A}{R_1 + R_2}$$

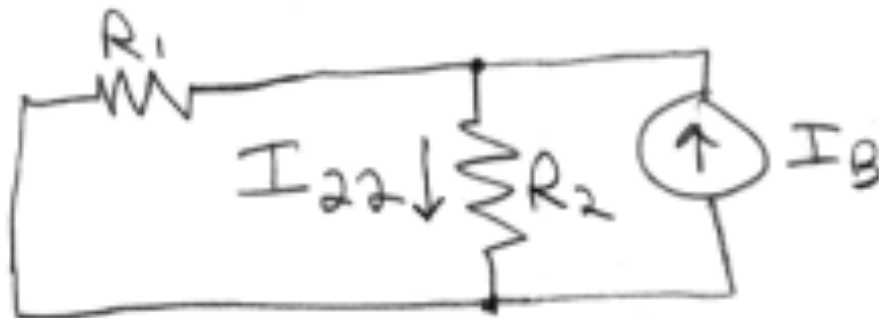


Setting  $V_A$  to zero (short circuit)

$$I_{22} = \frac{I_B R_1}{R_1 + R_2}$$

Add the two independent currents together:

$$I_2 = I_{21} + I_{22} = \frac{V_A + I_B R_1}{R_1 + R_2}$$

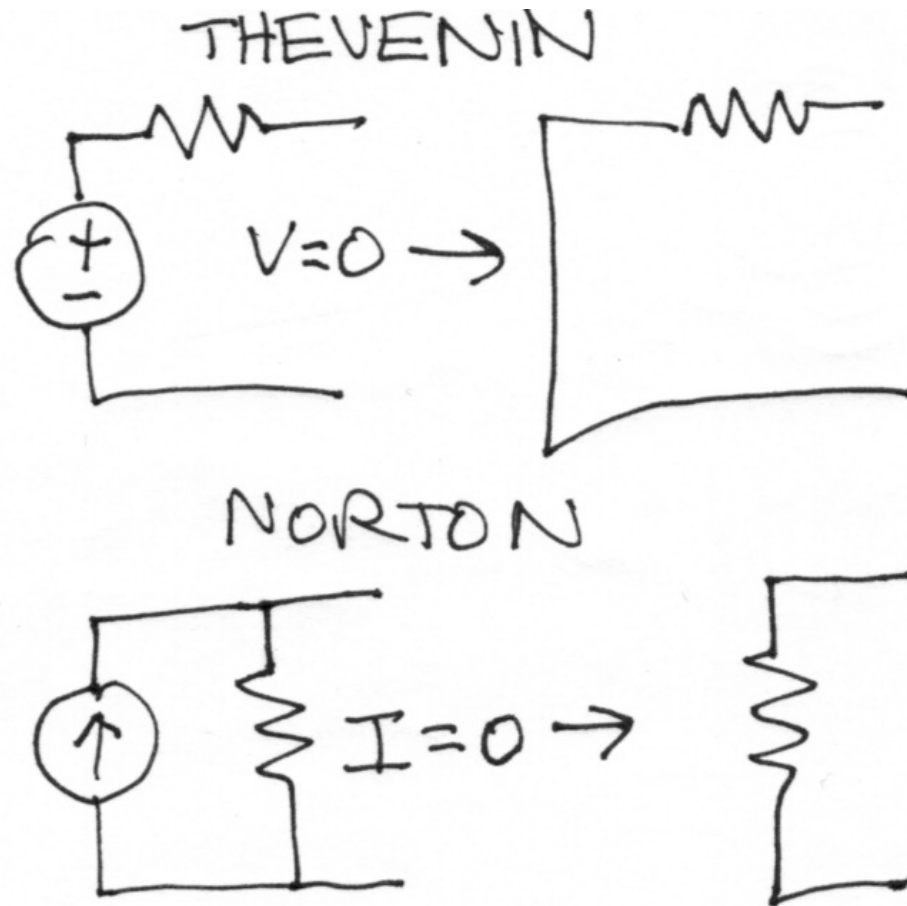
# Finding Thevenin/Norton Resistance, Using Superposition



- $R_{\text{Thevenin}} = R_{\text{Norton}}$  is the resistance when the voltage and current sources are set to 0.
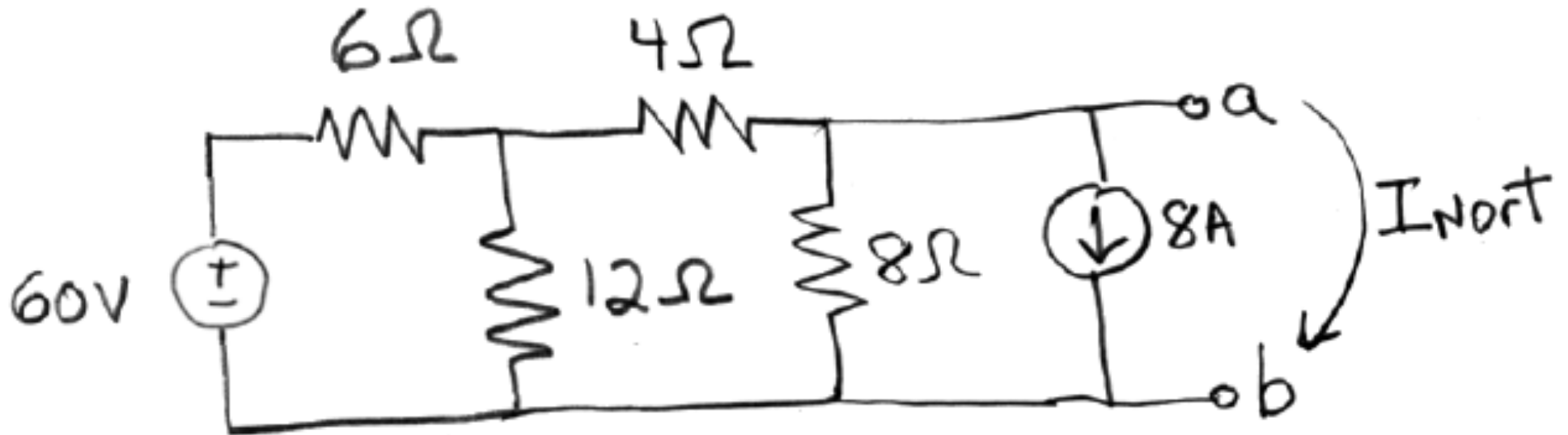
# Superposition Theorem – Another Example

Find Norton equivalent  $I_{\text{NORT}}$  from  $a$  to  $b$ ,  
and  $R_{\text{NORT}}$ , using Superposition.




$I_{\text{NORT}}$  is the current through a short circuit from  $a$  to  $b$ .

Break  $I_{NORT}$  into 2 components:

$$I_{NORT} = I_1 + I_2$$

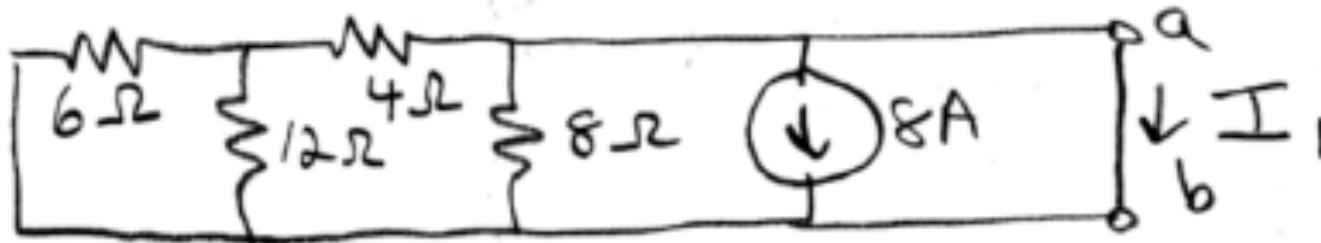
$I_1$  from current source with voltage source at 0V (short circuit).  
Ignore all resistors, since all current goes through short from  $a$  to  $b$ .



$$I_1 = -8A$$

current going  
the other way.

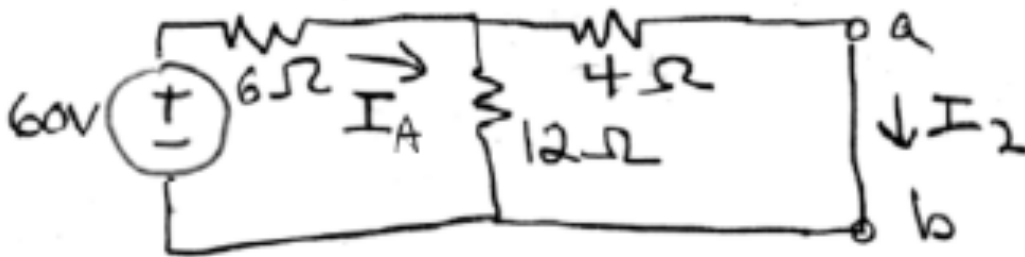$I_2$  from current source with current source at 0 A (open circuit).  
Ignore 8 Ω resistor since it is parallel to short from  $a$  to  $b$ .




$$I_A = 60 / (6 + (12 \times 4) / (12 + 4))$$

$$I_2 = I_A (12 / (12 + 4)) = 5A$$

$$I_{NORT} = I_1 + I_2 = -8A + 5A = -3A$$

To find  $R_{\text{NORT}}$  :

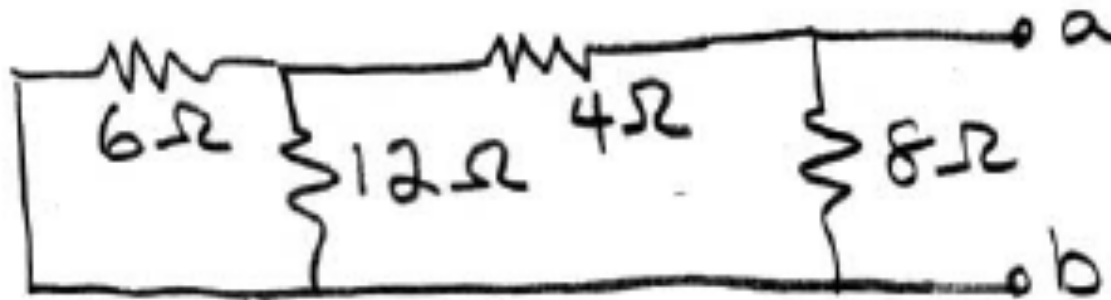- Set all voltage and current sources to 0 and find total resistance between  $a$  and  $b$ .
- This is  $R_{\text{NORT}}$  (which is the same as  $R_{\text{THEV}}$ )




simplify using parallel resistors  $(6 \times 12) / (6 + 12) = 4$




simplify further to two 8 ohm resistors in parallel, so

$$R_{\text{NORT}} = R_{\text{THEV}} = 4\Omega$$

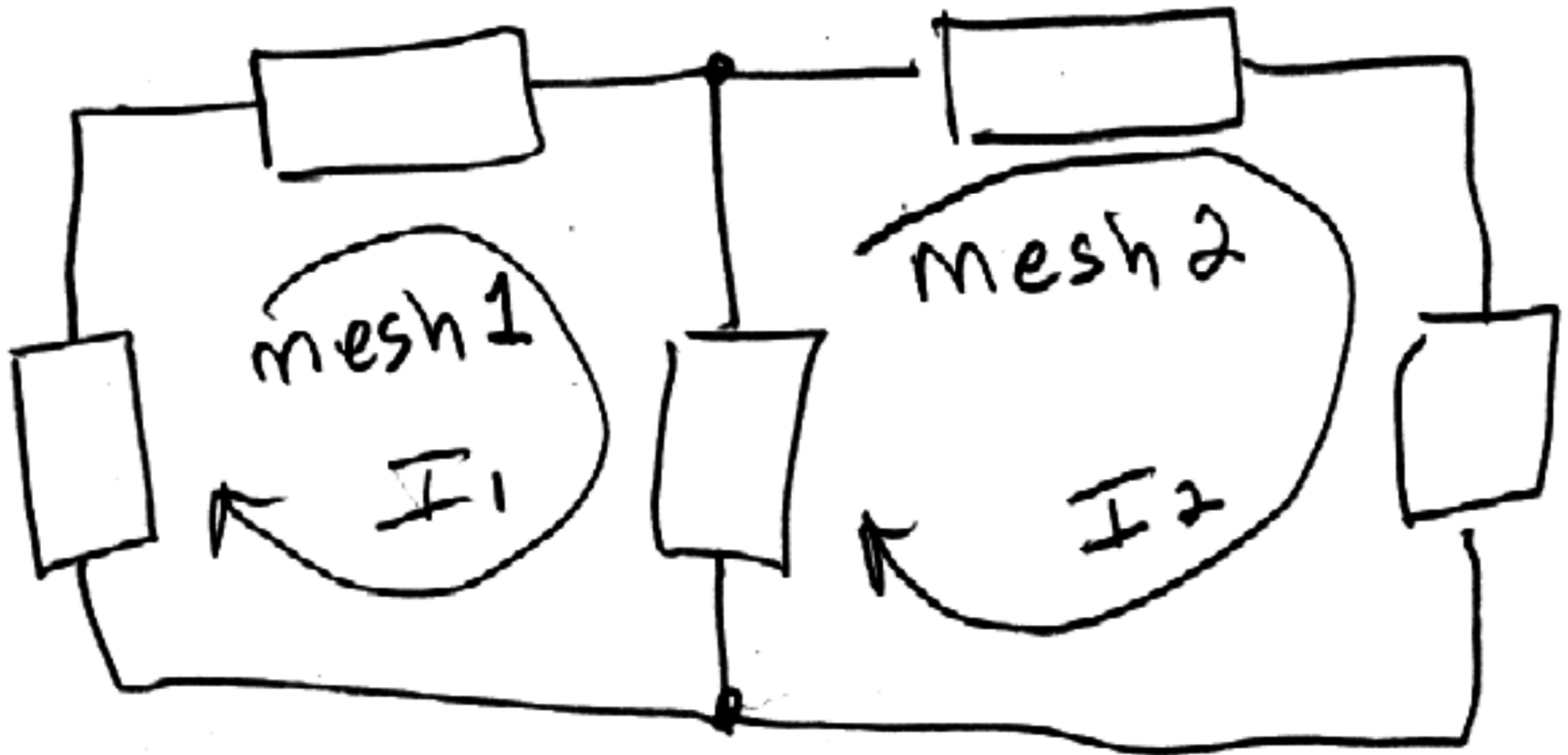Mesh analysis yield simultaneous linear equations.



# Example of a Mesh

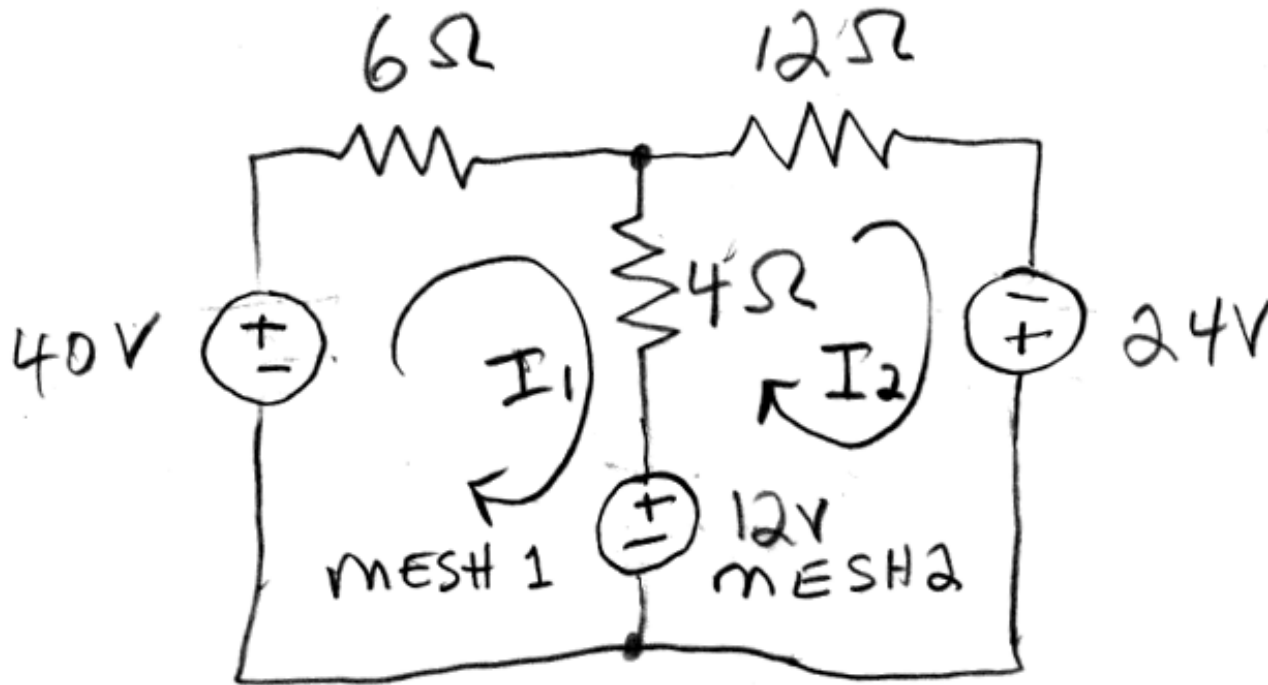


USING KIRCHHOFF'S VOLTAGE LAW

$$\begin{aligned} 10 I_1 - 4 I_2 &= 28 \\ -4 I_1 + 16 I_2 &= 36 \end{aligned}$$



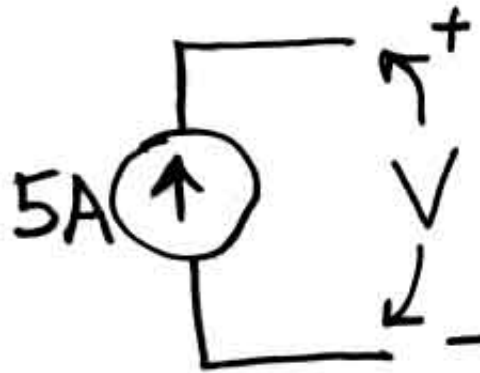
# DC Circuits without solutions

- There are basically 2 illegal DC circuits
  - Current source with open circuit:  $V = \infty$



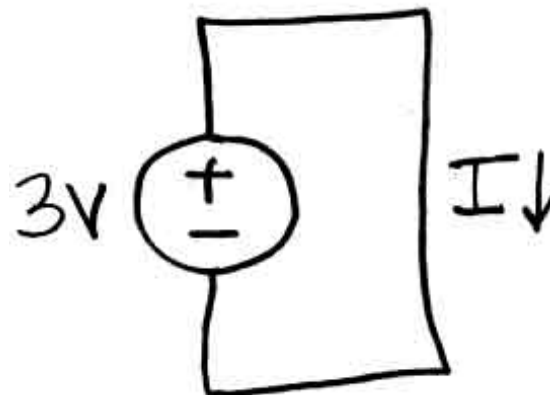
- Voltage source with short circuit:  $I = \infty$



# Analog Volt-Ohm-Meter (VOM)



# classic galvanometer (G)

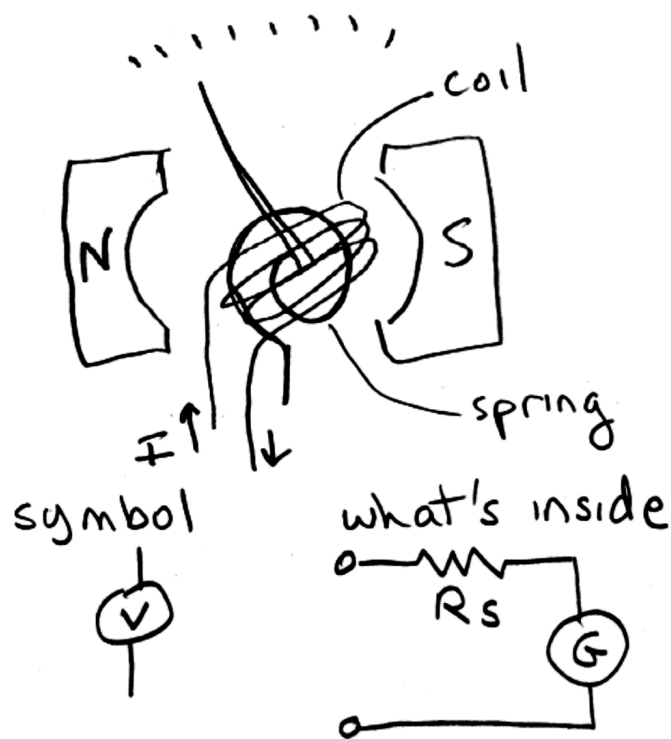

tiny current ( $50 \mu A$ )  
 through coil  
 moves needle  
 coil has  $\approx 0 \Omega$  resistance

voltmeter




your meter  
 $\downarrow$   
 $R_s$  is big,  $1 m\Omega - 1 g\Omega$   
 ("s" for series)

ammeter




$R_p$  is small  $< 1 \Omega$   
 ("p" for parallel)  
Easy to destroy meter!!

ohmmeter

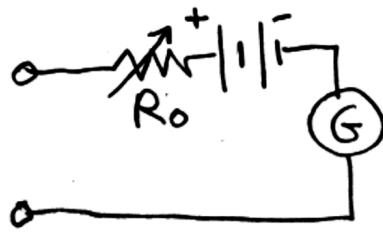

$R_o$  used to adjust  
 offset.  
 injects current...  
 only use on isolated,  
 non-powered resistors.

# Wheatstone Bridge

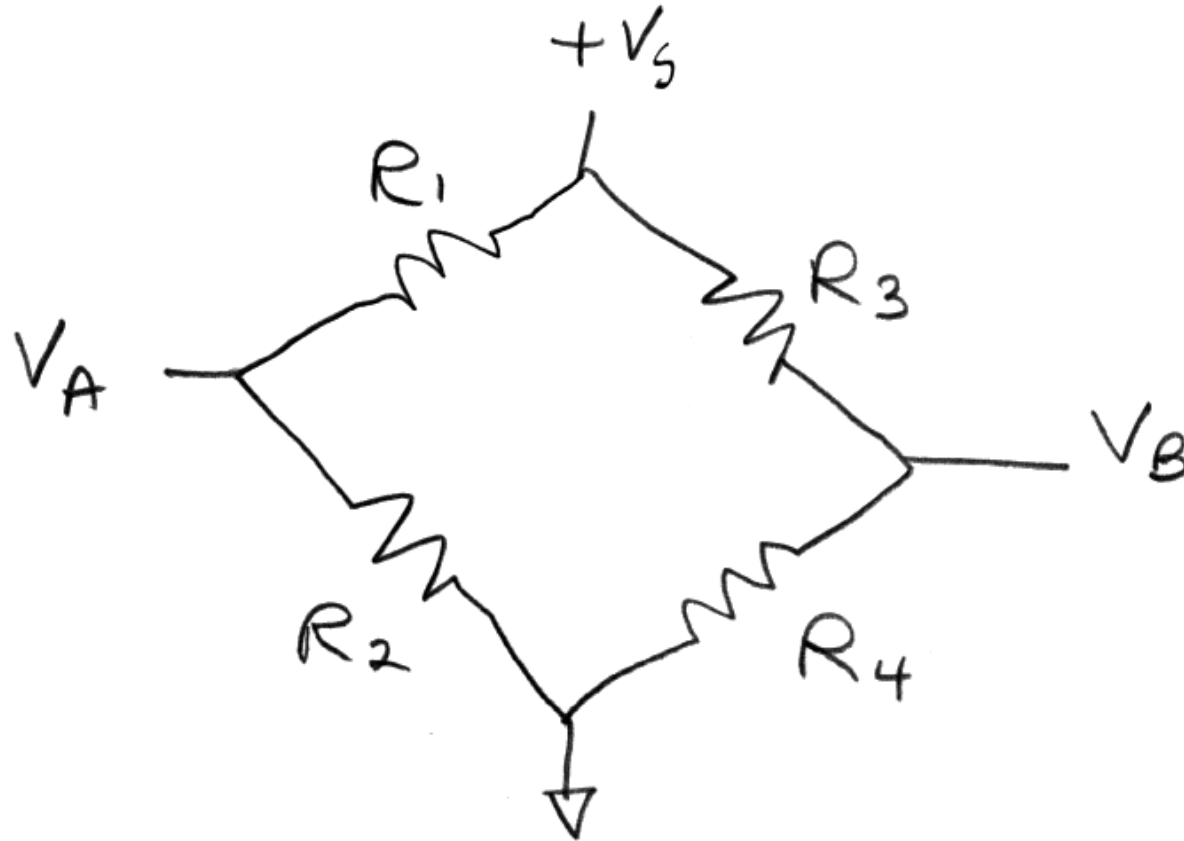

$$V_A = V_B \quad \text{when} \quad \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

- 2 voltage dividers

# Wheatstone Bridge

accurate measurement

setup

independent of  $V_s$




adjust  
pot so  
as to  
"zero"  
the  
voltmeter

- Like a mechanical balance for measuring weight
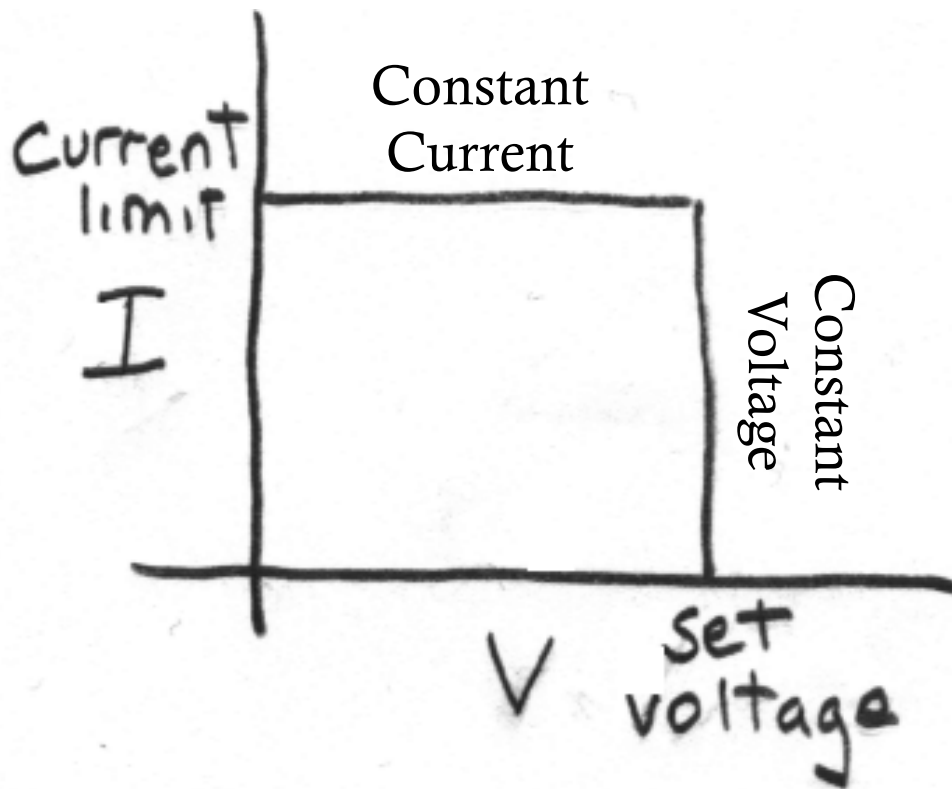
# Regulated Power Supply – Perfect but not Linear.

- It provides constant voltage (perfect voltage source) up to a certain current limit.
- Above that current limit, it provides constant current (perfect current source) but with a voltage that can drop to zero.
- Not a linear system.



set voltage & current limit



“CV”

*Constant Voltage*  
during normal  
operation.

“CC”

*Constant Current*  
when current  
limit is reached.

# Review of DC

- Constant perfect voltage and current sources, along with resistors, comprise circuits that produce a single solution (or no solution) based on linear simultaneous equations, in which each component obeys its own internal rule.
- Any branch made of the above components has a Thevenin and Norton equivalent. If the Thevenin/Norton resistance is non-zero, these represent real-world (non-perfect) voltage and current sources, respectively.
- Any branch consisting of only resistors can be simplified to a single resistor.